

Chapter 22 Organizer

Section/Objectives	Standards		Lab and Demo Planning
Chapter Opener	See page 14T for a key to the standards.		
	National	State/Local	
<p>Section 22.1</p> <ol style="list-style-type: none"> Describe conditions that create current in an electric circuit. Explain Ohm's law. Design closed circuits. Differentiate between power and energy in an electric circuit. 	UCP.1, UCP.2, UCP.3, A.1, A.2, B.6		<p>Student Lab: Launch Lab, p. 591: 1.5-V D-cell battery, insulated wire, flashlight bulb Additional Mini Lab, p. 595: vinegar or lemon juice, small pieces or disks of copper and zinc, alligator clip hookup wires (0–50 mm), voltmeter, paper towel Additional Mini Lab, p. 598: ammeter or multimeter, variable DC power supply, two lamps Mini Lab, p. 599: DC power supply (0–6 V), wires, two miniature lamps and sockets, ammeter</p> <p>Teacher Demonstration: Quick Demo, p. 597: variable DC power supply; two multimeters; 12-V lamp; lamp base or socket; 100-Ω, 2-W resistor; clip leads Quick Demo, p. 598: solar cell, amplifier, speaker, stroboscope</p>
<p>Section 22.2</p> <ol style="list-style-type: none"> Explain how electric energy is converted into thermal energy. Explore ways to deliver electric energy to consumers near and far. Define kilowatt-hour. 	UCP.1, UCP.2, UCP.3, A.1, A.2, B.6, E.1, F.1, F.3, F.4, F.6		<p>Student Lab: Physics Lab, pp. 606–607: four 1.5-V D batteries, four D-battery holders, one 10-kΩ resistor, one 500-μA ammeter, five wires with alligator clips, one 20-kΩ resistor, one 30-kΩ resistor, one 40-kΩ resistor</p> <p>Teacher Demonstration: Quick Demo, p. 603: 1-μF capacitor, 9-V battery, digital multimeter (DMV), 1-MΩ resistor</p>

Differentiated Instruction

L1 Level 1 activities should be appropriate for students with learning difficulties.

L2 Level 2 activities should be within the ability range of all students.

L3 Level 3 activities are designed for above-average students.

Reproducible Resources and Transparencies	Technology
<p>FAST FILE Chapters 21–25 Resources, Chapter 22 Transparency 22-1 Master, p. 55 Transparency 22-2 Master, p. 57 Transparency 22-3 Master, p. 59 Study Guide, pp. 43–48 Reinforcement, p. 51 Enrichment, pp. 53–54 Section 22-1 Quiz, p. 49 Mini Lab Worksheet, p. 37</p> <p> Teaching Transparency 22-1</p> <p> Teaching Transparency 22-2</p> <p> Teaching Transparency 22-3</p> <p>Connecting Math to Physics</p>	<p>TeacherWorks™ includes: Interactive Teacher Edition ■ Lesson Planner with Calendar ■ Access to all Blacklines ■ Correlation to Standards ■ Web links</p> <p> Interactive Chalkboard CD-ROM: Section 22.1 Presentation</p> <p> TeacherWorks™ CD-ROM</p> <p> Mechanical Universe: Simple DC Circuits</p>
<p>FAST FILE Chapters 21–25 Resources, Chapter 22 Transparency 22-4 Master, p. 61 Study Guide, pp. 43–48 Section 22-2 Quiz, p. 50 Physics Lab Worksheet, pp. 39–42</p> <p> Teaching Transparency 22-4</p> <p>Connecting Math to Physics Laboratory Manual, pp. 117–120 Probeware Laboratory Manual, pp. 41–44 Forensics Laboratory Manual, pp. 27–30</p>	<p> Interactive Chalkboard CD-ROM: Section 22.2 Presentation</p> <p> TeacherWorks™ CD-ROM</p> <p> Problem of the Week at physicspp.com</p>

Assessment Resources

<p>FAST FILE Chapters 21–25 Resources, Chapter 22 Chapter Assessment, pp. 63–68</p> <p>Additional Challenge Problems, p. 22 Physics Test Prep, pp. 43–44 Pre-AP/Critical Thinking, pp. 43–44 Supplemental Problems, pp. 43–44</p>	<p>Technology</p> <p> Interactive Chalkboard CD-ROM: Chapter 22 Assessment</p> <p> ExamView® Pro Testmaker CD-ROM</p> <p> Vocabulary PuzzleMaker</p> <p> TeacherWorks™ CD-ROM</p> <p> physicspp.com</p>
--	---

Chapter Overview

Current in electric circuits is discussed. Basic circuit components and their symbols are presented and used in schematic diagrams. Ohm's law is explained, as are power and the cost of using electric energy.

Think About This

Transmission at high voltage allows the required power to be delivered with minimum loss and with manageable wire sizes. See page 604 for more information about the transmission of electric energy.

► Key Terms

electric current, p. 592
conventional current, p. 592
battery, p. 592
electric circuit, p. 592
ampere, p. 593
resistance, p. 595
resistor, p. 596
parallel connection, p. 600
series connection, p. 600
superconductor, p. 603
kilowatt-hour, p. 605

What You'll Learn

- You will explain energy transfer in circuits.
- You will solve problems involving current, potential difference, and resistance.
- You will diagram simple electric circuits.

Why It's Important

The electric tools and appliances that you use are based upon the ability of electric circuits to transfer energy resulting from potential difference, and thus, perform work.

Power Transmission Lines Transmission lines crisscross our country to transfer energy to where it is needed. This transfer is accomplished at high potential differences, often as high as 500,000 V.

Think About This ►

Transmission line voltages are too high to use safely in homes and businesses. Why are such high voltages used in transmission lines?



physicspp.com

590

Lester Lefkowitz/CORBIS



LAUNCH Lab



Purpose Students should discover that there is electric current only when there is a complete loop for it to flow through.

Materials 1.5-V D-cell battery, insulated wire, flashlight bulb, protective eyewear

Teaching Strategies **CAUTION: Wire can scratch or cut skin.** Encourage students to record all their trials (diagram each of their circuits).

Recording the process of “trial & error” is part of the scientific process—Thomas Edison made many, many bulbs that did not work before finally identifying a material for the filament, which permitted him to make the lightbulb. Collecting data and information on all trials illustrates the importance of negative results in science. Scientists routinely learn a great deal from what others might commonly call their failures. It would have been a great waste of time if Edison had not kept track of the failures as he repeated his efforts.

LAUNCH Lab



Can you get a lightbulb to light?

Question

Given a wire, a battery, and a lightbulb, can you get the bulb to light?

Procedure

1. Obtain a lightbulb, a wire, and a battery. Try to find as many ways as possible to get the lightbulb to light. **Caution: Wire is sharp and can cut skin. Wire can also get hot if connected across the battery.**
2. Diagram two ways in which you are able to get the lightbulb to work. Be sure to label the battery, the wire, and the bulb.
3. Diagram at least three ways in which you are not able to get the bulb to light.

Analysis

How did you know if electric current was flowing? What do your diagrams of the lit bulb

have in common? What do your diagrams of the unlit bulb have in common? From your observations, what conditions seem to be necessary in order for the bulb to light?

Critical Thinking What causes electricity to flow through the bulb?



22.1 Current and Circuits

As you learned in Chapter 11, flowing water at the top of a waterfall has both potential and kinetic energy. However, the large amount of natural potential and kinetic energy available from resources such as Niagara Falls are of little use to people or manufacturers who are 100 km away, unless that energy can be transported efficiently. Electric energy provides the means to transfer large quantities of energy great distances with little loss. This transfer usually is done at high potential differences through power lines, such as those shown in the photo on the left. Once this energy reaches the consumer, it can easily be converted into another form or combination of forms, including sound, light, thermal energy, and motion.

Because electric energy can so easily be changed into other forms, it has become indispensable in our daily lives. Even quick glances around you will likely generate ample examples of the conversion of electric energy. Inside, lights to help you read at night, microwaves and electric ranges to cook food, computers, and stereos all rely on electricity for power. Outside, street lamps, store signs, advertisements, and the starters in cars all use flowing electric charges. In this chapter, you will learn how potential differences, resistance, and current are related. You also will learn about electric power and energy transfer.

Objectives

- **Describe** conditions that create current in an electric circuit.
- **Explain** Ohm's law.
- **Design** closed circuits.
- **Differentiate** between power and energy in an electric circuit.

Vocabulary

electric current
conventional current
battery
electric circuit
ampere
resistance
resistor
parallel connection
series connection

Section 22.1 Current and Circuits 591

Horizons Companies

Expected Results Students should find two main ways to light the bulb. In one way, the battery touches the bottom of the bulb; in the other way, it touches the side of the bulb. The bulb must touch the battery at a terminal, with the wire completing the circuit from the bulb's other contact point (side or bottom) to the battery's other terminal.

Analysis In order for electric charge to flow, there must be a closed circuit with an energy source in it. The battery is the energy source in this example. The lightbulb's bottom is one contact point,

and the bulb's side is the other contact point. If there is no battery or if the circuit does not go through both of the bulb's contacts, then the bulb will not light.

Critical Thinking Electric charges flow from one terminal on the battery through the wire, through the filament of the bulb, through the other wire to the other terminal.

1 FOCUS

Bellringer Activity

Power Connect a variable power supply to a 60-W lightbulb. Use the meters on the power supply or external multimeters to monitor voltage and current. Have students deliver increasing voltage to the lightbulb and calculate the power for several different voltages. Ask them to draw a conclusion about the relationship between the brightness of the bulb and the power, P . **The bulb will emit more light as the power increases. As the voltage increases, resistance remains constant, and power increases.**

L2 Visual-Spatial**Tie to Prior Knowledge**

Energy Students will apply what they have learned regarding the concept of energy transformation. They will also apply the definition of power that they explored in their study of mechanics to electric devices.

**PowerPoint® Presentations**

This CD-ROM is an editable Microsoft® PowerPoint® presentation that includes:

- Section presentations
- Interactive graphics
- Image bank
- All transparencies
- Audio reinforcement
- All new Section and Chapter Assessment questions
- Links to physicspp.com

2 TEACH

Identifying Misconceptions

Language It is not a good idea to use phrases such as “the voltage through this circuit.” Students must realize that voltage is always measured as a potential difference across two points. Charges move through a circuit—not voltage and not current. It is fine to discuss the voltage in a circuit when it’s clear what the reference points are.

Using an Analogy

Current Ask students to describe how electric currents are similar to water currents. **Current itself doesn’t flow, but water and charges flow. Ask students to provide their own analogy to describe a circuit or current (for example, model train tracks).** L2

Critical Thinking

Battery Chargers Using what students have learned about potential differences and the flow of charges, ask them to explain how a cell phone battery is recharged by plugging it into an electrical outlet. Ask them if this is different from when it is plugged into an automobile’s cigarette lighter. **Preliminary discussion on this point will include the flow of electrons from the car battery or from the household power system into the object being charged. This point can be revisited and expanded later when students are discussing batteries and chemical energy, and again when AC/DC power conversion is presented.** L3

Producing Electric Current

In Chapter 21, you learned that when two conducting spheres touch, charges flow from the sphere at a higher potential to the one at a lower potential. The flow continues until there is no potential difference between the two spheres.

A flow of charged particles is an **electric current**. In **Figure 22-1a**, two conductors, A and B, are connected by a wire conductor, C. Charges flow from the higher potential difference of B to A through C. This flow of positive charge is called **conventional current**. The flow stops when the potential difference between A, B, and C is zero. You could maintain the electric potential difference between B and A by pumping charged particles from A back to B, as illustrated in **Figure 22-1b**. Since the pump increases the electric potential energy of the charges, it requires an external energy source to run. This energy could come from a variety of sources. One familiar source, a voltaic or galvanic cell (a common dry cell), converts chemical energy to electric energy. Several galvanic cells connected together are called a **battery**. A second source of electric energy—a photovoltaic cell, or solar cell—changes light energy into electric energy.

Electric Circuits


The charges in Figure 22-1b move around a closed loop, cycling from the pump to B, through C, to A and back to the pump. Any closed loop or conducting path allowing electric charges to flow is called an **electric circuit**. A circuit includes a charge pump, which increases the potential energy of the charges flowing from A to B, and a device that reduces the potential energy of the charges flowing from B to A. The potential energy lost by the charges, qV , moving through the device is usually converted into some other form of energy. For example, electric energy is converted to kinetic energy by a motor, to light energy by a lamp, and to thermal energy by a heater.

A charge pump creates the flow of charged particles that make up a current. Consider a generator driven by a waterwheel, such as the one pictured in **Figure 22-2a**. The water falls and rotates the waterwheel and generator. Thus, the kinetic energy of the water is converted to electric energy by the generator. The generator, like the charge pump, increases the electric potential difference, V . Energy in the amount qV is needed to increase the potential difference of the charges. This energy comes from the change in energy of the water. Not all of the water’s kinetic energy, however, is converted to electric energy, as shown in **Figure 22-2b**.

If the generator attached to the waterwheel is connected to a motor, the charges in the wire flow into the motor. The flow of charges continues through the circuit back to the generator. The motor converts electric energy to kinetic energy.

Conservation of charge Charges cannot be created or destroyed, but they can be separated. Thus, the total amount of charge—the number of negative electrons and positive ions—in the circuit does not change. If one coulomb flows through the generator in 1 s, then one coulomb also will flow through the motor in 1 s. Thus, charge is a conserved quantity. Energy also is conserved. The change in electric energy, ΔE , equals qV . Because q is conserved,

■ **Figure 22-1** Conventional current is defined as positive charges flowing from the positive plate to the negative plate (**a**). A generator pumps the positive charges back to the positive plate and maintains the current (**b**). In most metals, negatively-charged electrons actually flow from the negative to the positive plate, creating the appearance of positive charges that are moving in the opposite direction.

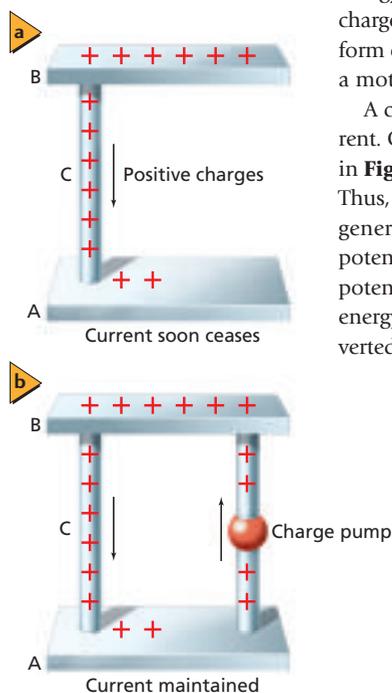

592 Chapter 22 Current Electricity

22.1 Resource MANAGER

FAST FILE Chapters 21–25 Resources

Transparency 22-1 Master, p. 55
Transparency 22-2 Master, p. 57
Transparency 22-3 Master, p. 59
Study Guide, pp. 43–44
Reinforcement, p. 51
Enrichment, pp. 53–54
Section 22-1 Quiz, p. 49
Mini Lab Worksheet, p. 37

Teaching Transparency 22-1


Teaching Transparency 22-2
Teaching Transparency 22-3
Connecting Math to Physics

Technology

TeacherWorks™ CD-ROM
Interactive Chalkboard CD-ROM
ExamView® Pro Testmaker CD-ROM

physicspp.com

physicspp.com/vocabulary_puzzlemaker

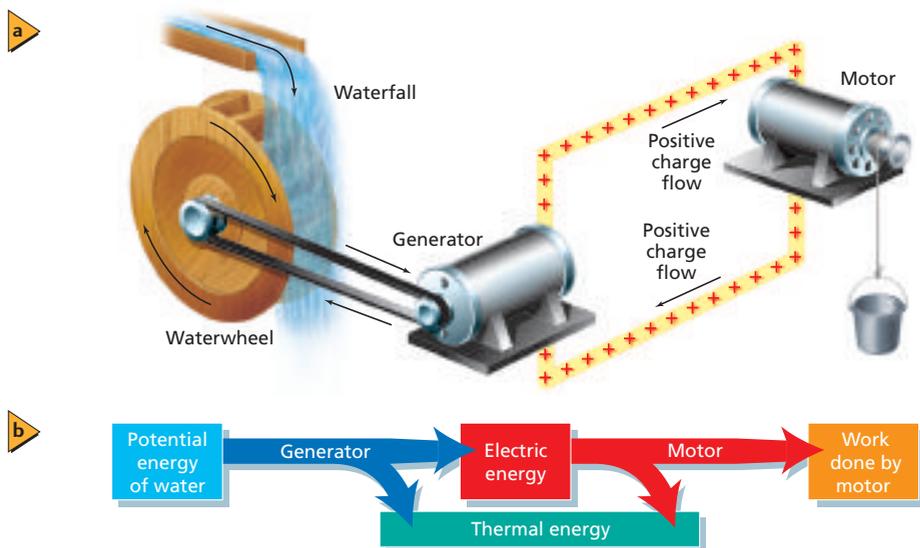

■ **Figure 22-2** The potential energy of the waterfall is eventually converted into work done on the bucket (a). The production and use of electric current is not 100 percent efficient. Some thermal energy is produced by the splashing water, friction, and electric resistance (b).

the net change in potential energy of the charges going completely around the circuit must be zero. The increase in potential difference produced by the generator equals the decrease in potential difference across the motor.

If the potential difference between two wires is 120 V, the waterwheel and the generator must do 120 J of work on each coulomb of charge that is delivered. Every coulomb of charge moving through the motor delivers 120 J of energy to the motor.

Rates of Charge Flow and Energy Transfer

Power, which is defined in watts, W, measures the rate at which energy is transferred. If a generator transfers 1 J of kinetic energy to electric energy each second, it is transferring energy at the rate of 1 J/s, or 1 W. The energy carried by an electric current depends on the charge transferred, q , and the potential difference across which it moves, V . Thus, $E = qV$. Recall from Chapter 20 that the unit for the quantity of electric charge is the coulomb. The rate of flow of electric charge, q/t , called electric current, is measured in coulombs per second. Electric current is represented by I , so $I = q/t$. A flow of 1 C/s is called an **ampere**, A.

The energy carried by an electric current is related to the voltage, $E = qV$. Since current, $I = q/t$, is the rate of charge flow, the power, $P = E/t$, of an electric device can be determined by multiplying voltage and current. To derive the familiar form of the equation for the power delivered to an electric device, you can use $P = E/t$ and substitute $E = qV$ and $q = It$.

Power $P = IV$

Power is equal to the current times the potential difference.

If the current through the motor in Figure 22-2a is 3.0 A and the potential difference is 120 V, the power in the motor is calculated using the expression $P = (3.0 \text{ C/s})(120 \text{ J/C}) = 360 \text{ J/s}$, which is 360 W.

Using Figure 22-2

Ask students to use the general theme shown in the figure to describe the operation of car headlights, starting with the gasoline in the tank. **L1**

Concept Development

Current The following analogy will help students visualize the flow of electric charge, known as current. A beach resort uses a water tank to supply its needs. Too many guests take showers in the late afternoon, and many of them complain about the weak water flow. Ask students how the resort could alleviate this problem. **Raising the tank elevation would increase the water's potential energy, and larger pipes would decrease resistance.** Alternatively, ask students to think of the flow of electric charges (that is, current) as if it were traffic on a highway at rush hour. Ask how you could increase the flow of cars.

You could lower the resistance by widening the roadway and adding additional lanes, removing obstacles such as stoplights, or adding more exit ramps. You could increase the energy by raising the speed limit.

L2

THE MECHANICAL UNIVERSE

HIGH SCHOOL ADAPTATION



Videotape

Simple DC Circuits

HELPING STRUGGLING STUDENTS

Activity

Students Helping Students Some students have ways of explaining difficult concepts that other students find appealing. If students seem to struggle with a concept, try forming small discussion groups. Seed the discussions with questions such as the following: Why is a complete circuit necessary for charges to flow? Why is an energy source necessary for charges to flow? Describe resistance and voltage using everyday terms. What do voltage and pressure have in common? **L1 Interpersonal**

▶ IN-CLASS Example

Question A 120-V motor operates at 13 A. Determine the power and the energy used in one hour of operation.



Answer $P = IV$, $P = 120 \text{ V} \times 13 \text{ A}$,
 $P = 1.6 \text{ kW}$; $E = Pt$, $E = 1.6 \text{ kJ/s} \times$
 $60 \text{ min} \times 60 \text{ sec/min}$, $E = 5.8 \text{ MJ}$



ACTIVITY

■ Energy and the Environment

Ask students to investigate why wasting electric energy has a negative environmental impact. Suggest they list some examples of personal, national, and school activities that could be wasting electric energy and then provide solutions to reduce the waste.

L2 Linguistic

▶ PRACTICE Problems

- 63 W
- 24 W
- 0.60 A
- $2.5 \times 10^4 \text{ J}$
- 0.30 A

Identifying Misconceptions

Resistance v. Resistivity While it is accurate to talk about the resistance in a copper wire, it does not make sense to talk about the resistance of the copper itself because resistance changes with both length and cross-sectional area. Because resistance is inversely proportional to a cross-sectional area and directly proportional to length, resistivity can be determined by multiplying resistance in a wire by the wire's area and dividing by the wire's length: $\Omega (\text{m}^2/\text{m}) = \Omega \cdot \text{m}$.


▶ EXAMPLE Problem 1

Electric Power and Energy A 6.0-V battery delivers a 0.50-A current to an electric motor connected across its terminals.

- What power is delivered to the motor?
- If the motor runs for 5.0 min, how much electric energy is delivered?

1 Analyze and Sketch the Problem

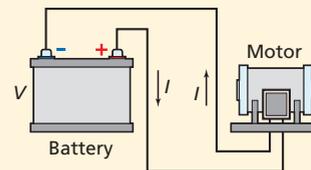- Draw a circuit showing the positive terminal of a battery connected to a motor and the return wire from the motor connected to the negative terminal of the battery.
- Show the direction of conventional current.



Known: $V = 6.0 \text{ V}$
 $I = 0.50 \text{ A}$
 $t = 5.0 \text{ min}$

Unknown: $P = ?$
 $E = ?$

2 Solve for the Unknown

- Use $P = IV$ to find the power.

$$P = IV$$

$$P = (0.50 \text{ A})(6.0 \text{ V})$$

$$= 3.0 \text{ W}$$

Substitute $I = 0.50 \text{ A}$, $V = 6.0 \text{ V}$

- In Chapter 10, you learned that $P = E/t$. Solve for E to find the energy.

$$E = Pt$$

$$= (3.0 \text{ W})(5.0 \text{ min})$$

Substitute $P = 3.0 \text{ W}$, $t = 5.0 \text{ min}$

$$= (3.0 \text{ J/s})(5.0 \text{ min}) \left(\frac{60 \text{ s}}{1 \text{ min}} \right)$$

$$= 9.0 \times 10^2 \text{ J}$$

Math Handbook

Significant Digits
page 834

3 Evaluate the Answer

- Are the units correct?** Power is measured in watts, and energy is measured in joules.
- Is the magnitude realistic?** With relatively low voltage and current, a few watts of power is reasonable.

▶ PRACTICE Problems




Additional Problems, Appendix B

- The current through a lightbulb connected across the terminals of a 125-V outlet is 0.50 A. At what rate does the bulb convert electric energy to light? (Assume 100 percent efficiency.)
- A car battery causes a current of 2.0 A through a lamp and produces 12 V across it. What is the power used by the lamp?
- What is the current through a 75-W lightbulb that is connected to a 125-V outlet?
- The current through the starter motor of a car is 210 A. If the battery maintains 12 V across the motor, how much electric energy is delivered to the starter in 10.0 s?
- A flashlight bulb is rated at 0.90 W. If the lightbulb drops 3.0 V, how much current goes through it?

DIFFERENTIATED INSTRUCTION

Activity

Hearing Impaired The Bellringer Activity with the battery and the lightbulb may also be performed with a battery and an electric bell (doorbell) or a buzzer. Additionally, you could demonstrate how to replace the bell on a door with a flashing light as is done for hearing-impaired individuals or in a soundproof location (such as a recording studio). Note: A variety of personal electronic devices exist to assist visually impaired individuals. Some students in your class may possess PDAs that are capable of scanning written text and translating it into Braille, or ones that access an audible speech synthesizer. **L1**

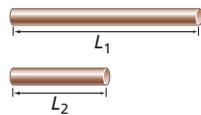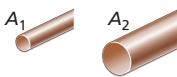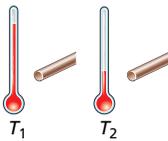Table 22-1		
Changing Resistance		
Factor	How resistance changes	Example
Length	Resistance increases as length increases.	 $R_{L1} > R_{L2}$
Cross-sectional area	Resistance increases as cross-sectional area decreases.	 $R_{A1} > R_{A2}$
Temperature	Resistance increases as temperature increases.	 $R_{T1} > R_{T2}$
Material	Keeping length, cross-sectional area, and temperature constant, resistance varies with the material used.	 Platinum Iron Aluminum Gold Copper Silver

Resistance and Ohm's Law


Suppose two conductors have a potential difference between them. If they are connected with a copper rod, a large current is created. On the other hand, putting a glass rod between them creates almost no current. The property determining how much current will flow is called **resistance**. **Table 22-1** lists some of the factors that impact resistance. Resistance is measured by placing a potential difference across a conductor and dividing the voltage by the current. The resistance, R , is defined as the ratio of electric potential difference, V , to the current, I .

$$\text{Resistance } R = \frac{V}{I}$$

Resistance is equal to voltage divided by current.

The resistance of the conductor, R , is measured in ohms. One ohm (1Ω) is the resistance permitting an electric charge of 1 A to flow when a potential difference of 1 V is applied across the resistance. A simple circuit relating resistance, current, and voltage is shown in **Figure 22-3**. A 12-V car battery is connected to one of the car's $3\text{-}\Omega$ brake lights. The circuit is completed by a connection to an ammeter, which is a device that measures current. The current carrying the energy to the lights will measure 4 A .

■ **Figure 22-3** One ohm, Ω , is defined as 1 V/A . In a circuit with a $3\text{-}\Omega$ resistance and a 12-V battery, there is a 4-A current.

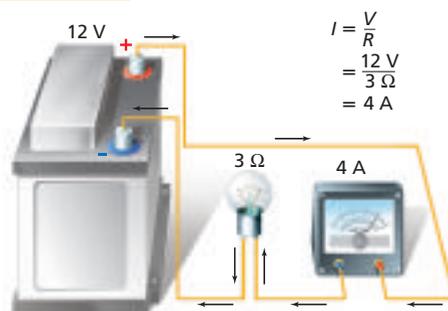

Section 22.1 Current and Circuits 595

Discussion

Question To begin the discussion, show students a D cell and an AAA cell. Point out that both are rated at 1.5 V and ask students to describe the significant difference between them.

Answer The D cell will last longer with a given load. Because the D cell has more mass (and consequently more chemicals), it can supply a given current for a longer period of time before the chemical energy is depleted. **L1**

Additional MINI LAB

Making Electric Energy



Purpose to observe electric energy from a series of cells

Materials vinegar or lemon juice, small pieces or disks of copper and zinc, alligator clip hookup wires (0 to 50 mm), voltmeter, paper towel

Procedure

CAUTION: Wear protective eyewear.

- Place a small piece of folded, vinegar-soaked paper towel between a piece of copper and zinc.
- Attach the voltmeter to the copper and the zinc. Measure the potential difference.
- Make several more cells of copper, vinegar-soaked paper-towel electrolyte, and zinc. Carefully make a series circuit by placing a copper piece against a zinc piece. Again, measure the potential difference from the top copper piece to the bottom zinc piece in your stack.
- Wire the ammeter in series with the cells and determine if you have current. Each cell's potential difference is about 0.1 V .

Assessment Ask students how this method of generating electricity is superior to electricity generated by using wool and a rubber rod. **The cells generate an electric current, while the static electricity generated by the other method is intermittent.** Ask students to identify the load in the circuit (there was no designated resistor used in the demonstration). **The ammeter was acting as a load.**

Teacher F.Y.I.

CONTENT BACKGROUND


Resistors Resistors are made to create a precise quantity of resistance for insertion into a circuit. They are typically constructed of metal wire or carbon, and engineered to maintain a stable resistance value over a wide range of environmental conditions. Unlike lamps, they do not produce light, but they do produce heat as electric power is dissipated by them in a working circuit. Typically, though, the purpose of a resistor is not to produce usable heat, but simply to provide a precise quantity of electrical resistance. Because resistors dissipate heat energy as the electric currents through them overcome the "friction" of their resistance, resistors are also rated in terms of how much heat energy they can dissipate without overheating and sustaining damage.

Using an Analogy

Resistance and Walking To make the concept of resistance more concrete, try comparing electric resistance to the resistance a person might experience walking over different surfaces. Walking on asphalt is very easy (low resistance), walking across a muddy field is a bit more difficult, and walking through crowded hallways is extremely difficult (high resistance).



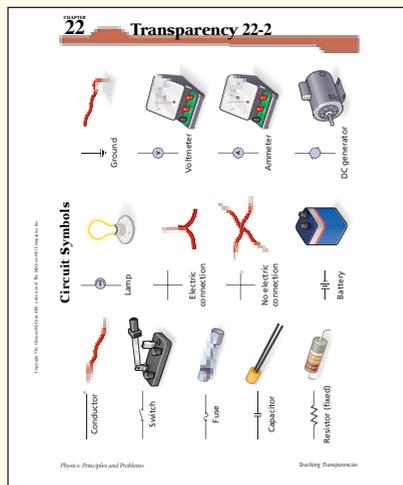
Page 55, **FAST FILE**
Chapters 21–25 Resources



Reinforcement

Completing the Circuit Ask students to identify these items: (1) they support the flow of charge (current) in wires, (2) a chemical charge pump, (3) converts electric energy to heat, (4) converts electric energy to mechanical energy, (5) converts mechanical energy to electricity, (6) a law that states that the relationship between potential difference and current is a constant for a given conductor, and (7) the rate of converting energy.

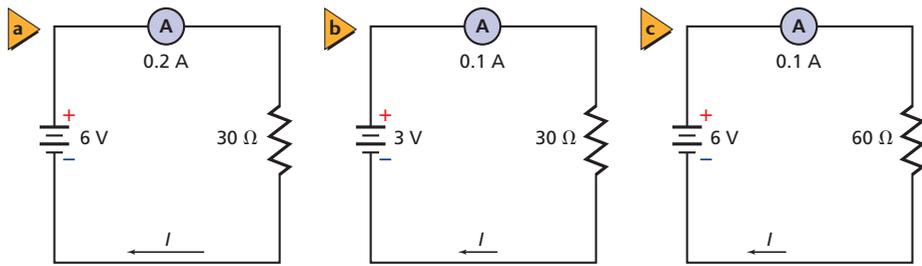- (1) electrons, (2) battery or cell, (3) resistance or resistor, (4) motor, (5) generator, (6) Ohm's law, (7) power **L1 Linguistic**



■ **Figure 22-4** The current through a simple circuit (a) can be regulated by removing some of the dry cells (b) or by increasing the resistance of the circuit (c).


The unit for resistance is named for German scientist Georg Simon Ohm, who found that the ratio of potential difference to current is constant for a given conductor. The resistance for most conductors does not vary as the magnitude or direction of the potential applied to it changes. A device having constant resistance independent of the potential difference obeys Ohm's law.

Most metallic conductors obey Ohm's law, at least over a limited range of voltages. Many important devices, however, do not. A radio and a pocket calculator contain many devices, such as transistors and diodes, that do not obey Ohm's law. Even a lightbulb has resistance that depends on its temperature and does not obey Ohm's law.

Wires used to connect electric devices have low resistance. A 1-m length of a typical wire used in physics labs has a resistance of about 0.03Ω . Wires used in home wiring offer as little as 0.004Ω of resistance for each meter of length. Because wires have so little resistance, there is almost no potential drop across them. To produce greater potential drops, a large resistance concentrated into a small volume is necessary. A **resistor** is a device designed to have a specific resistance. Resistors may be made of graphite, semiconductors, or wires that are long and thin.

There are two ways to control the current in a circuit. Because $I = V/R$, I can be changed by varying V , R , or both. **Figure 22-4a** shows a simple circuit. When V is 6 V and R is 30Ω , the current is 0.2 A . How could the current be reduced to 0.1 A ? According to Ohm's law, the greater the voltage placed across a resistor, the larger the current passing through it. If the current through a resistor is cut in half, the potential difference also is cut

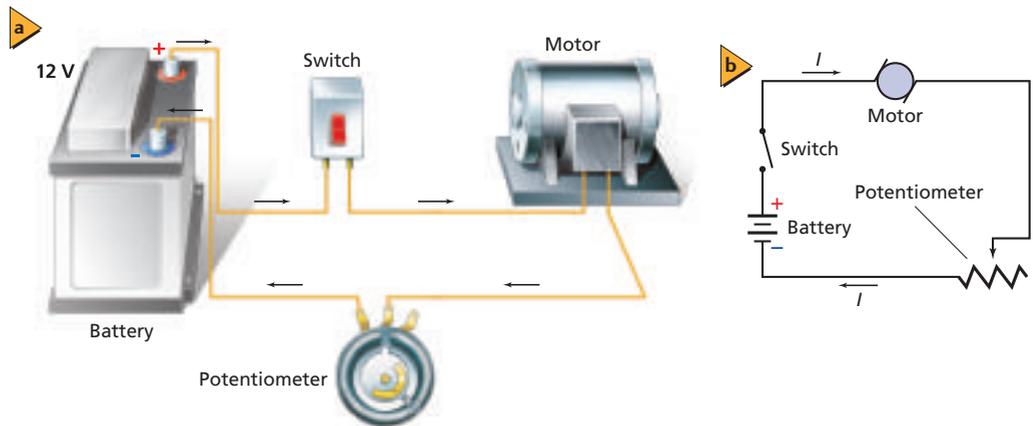■ **Figure 22-5** A potentiometer can be used to change current in an electric circuit.



596 Chapter 22 Current Electricity

Teacher F.Y.I.

REAL-LIFE PHYSICS

Resistance and Resistivity Engineers use resistivity to predict resistance. Imagine current running through a copper wire that is 2.0 m in length and 2.0 mm in diameter. To predict the resistance of the wire, you can use the formula $R = \rho L/A$, where R is the resistance in ohms, ρ is the resistivity of copper in Ω -meters, L is the length in meters, and A is the cross-sectional area in square meters. Substituting the appropriate values gives

$$R = \rho L/A = \frac{(1.68 \times 10^{-8} \Omega \cdot \text{m})(2.0 \text{ m})}{\pi(1.0 \times 10^{-3} \text{ m})^2} = 1.1 \times 10^{-2} \Omega$$


in half. In **Figure 22-4b**, the voltage applied across the resistor is reduced from 6 V to 3 V to reduce the current to 0.1 A. A second way to reduce the current to 0.1 A is to replace the 30-Ω resistor with a 60-Ω resistor, as shown in **Figure 22-4c**.

Resistors often are used to control the current in circuits or parts of circuits. Sometimes, a smooth, continuous variation of the current is desired. For example, the speed control on some electric motors allows continuous, rather than step-by-step, changes in the rotation of the motor. To achieve this kind of control, a variable resistor, called a potentiometer, is used. A circuit containing a potentiometer is shown in **Figure 22-5**. Some variable resistors consist of a coil of resistance wire and a sliding contact point. Moving the contact point to various positions along the coil varies the amount of wire in the circuit. As more wire is placed in the circuit, the resistance of the circuit increases; thus, the current changes in accordance with the equation $I = V/R$. In this way, the speed of a motor can be adjusted from fast, with little wire in the circuit, to slow, with a lot of wire in the circuit. Other examples of using variable resistors to adjust the levels of electrical energy can be found on the front of a TV: the volume, brightness, contrast, tone, and hue controls are all variable resistors.

The human body The human body acts as a variable resistor. When dry, skin's resistance is high enough to keep currents that are produced by small and moderate voltages low. If skin becomes wet, however, its resistance is lower, and the electric current can rise to dangerous levels. A current as low as 1 mA can be felt as a mild shock, while currents of 15 mA can cause loss of muscle control and currents of 100 mA can cause death.

Diagramming Circuits

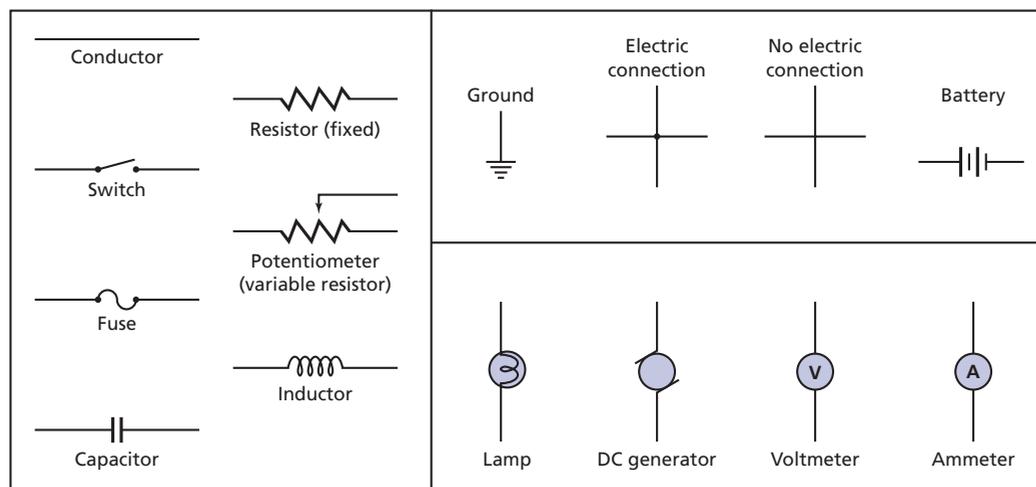A simple circuit can be described in words. It can also be depicted by photographs or artists' drawings of the parts. Most frequently, however, an electric circuit is drawn using standard symbols for the circuit elements. Such a diagram is called a circuit schematic. Some of the symbols used in circuit schematics are shown in **Figure 22-6**.



APPLYING PHYSICS

► **Resistance** The resistance of an operating 100-W lightbulb is about 140 Ω. When the lightbulb is turned off and at room temperature, its resistance is only about 10 Ω. This is because of the great difference between room temperature and the lightbulb's operating temperature. ◀

Biology Connection

APPLYING PHYSICS

► Calculate the current and power at the moment that a room-temperature 100-W bulb is turned on. $I = V/R = 120 \text{ V}/10 \text{ } \Omega = 10 \text{ A}$. $P = IV = (10 \text{ A})(120 \text{ V}) = 1 \text{ kW}$. This represents a rather large initial heating effect. If possible, obtain a clear 100-W bulb so that students can see the size of the filament. ◀

QUICK DEMO

Ohm's Law

Estimated Time 10 minutes

Materials variable DC power supply, multimeters (2), 12-V lamp, lamp base or socket (as needed), 100-Ω, 2-W resistor, clip leads

Procedure Connect the circuit as shown in Figure 22-7, using the power supply rather than a battery. Start at 0 V and ask a student assistant to record the voltage and current on the chalkboard. Increase the power supply output in 2-V steps until 12 V is reached. Have the assistant record the voltage and current at each step. Have a second student assistant draw a graph on the chalkboard. Repeat the entire process using the resistor in place of the lamp. Lead a class discussion using Ohm's law as the focus.

■ **Figure 22-6** These symbols commonly are used to diagram electric circuits.

Teacher F.Y.I.

CONTENT BACKGROUND

Temperature and Resistance Almost all conductors have a positive temperature coefficient of resistivity, α . The temperature coefficient of resistivity can be determined by an equation similar to that for the coefficient of linear expansion (Chapter 13). The following formula can be used to

predict the change in resistance: $R_1 = R_2 \left(\frac{1 + \alpha T_1}{1 + \alpha T_2} \right)$. R_1 is the resistance in Ω at temperature

T_1 in °C, R_2 is the resistance in Ω at temperature T_2 in °C, and α is the temperature coefficient of resistivity in (°C)⁻¹.

▶ IN-CLASS Example

Question A 9.0-V battery is connected to a 15-k Ω resistor. What is the current in this circuit?



Answer

$$I = \frac{V}{R} = \frac{9.0 \text{ V}}{15 \text{ k}\Omega} = 0.60 \text{ mA}$$

Additional MINI LAB

Measuring Current



Purpose to connect an ammeter and observe current at all points in a series circuit

Materials ammeter or multimeter, variable DC power supply, two lamps

Procedure Connect a variable DC power supply and two lamps in series. Use a multimeter or an ammeter to measure the current at each place where the circuit can be opened and the meter inserted.

Assessment What is the correct method of connecting an ammeter? **in series** Draw a conclusion about the current at various points in a series circuit. **It is the same.**

▶ PRACTICE Problems

6. 0.36 A
7. $1.2 \times 10^2 \text{ V}$
8. $1.5 \times 10^4 \Omega$
9. a. $2.4 \times 10^2 \Omega$
b. $6.0 \times 10^1 \text{ W}$
10. a. 0.60 A
b. $2.1 \times 10^2 \Omega$
11. a. $6.3 \times 10^1 \text{ V}$
b. $2.1 \times 10^2 \Omega$
c. 19 W

▶ EXAMPLE Problem 2

Current Through a Resistor A 30.0-V battery is connected to a 10.0- Ω resistor. What is the current in the circuit?

1 Analyze and Sketch the Problem

- Draw a circuit containing a battery, an ammeter, and a resistor.
- Show the direction of the conventional current.

Known: $V = 30.0 \text{ V}$

$$R = 10.0 \Omega$$

Unknown: $I = ?$


2 Solve for the Unknown

Use $I = V/R$ to determine the current.

$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{30.0 \text{ V}}{10.0 \Omega} \quad \text{Substitute } V = 30.0 \text{ V, } R = 10.0 \Omega \\ &= 3.00 \text{ A} \end{aligned}$$

3 Evaluate the Answer

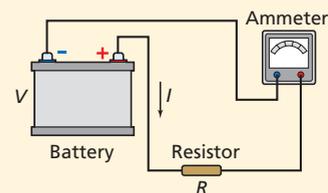- **Are the units correct?** Current is measured in amperes.
- **Is the magnitude realistic?** There is a fairly large voltage and a small resistance, so a current of 3.00 A is reasonable.



Math Handbook

Operations with Significant Digits
pages 835–836

▶ PRACTICE Problems Additional Problems, Appendix B

For all problems, assume that the battery voltage and lamp resistances are constant, no matter what current is present.

6. An automobile panel lamp with a resistance of 33 Ω is placed across a 12-V battery. What is the current through the circuit?
7. A motor with an operating resistance of 32 Ω is connected to a voltage source. The current in the circuit is 3.8 A. What is the voltage of the source?
8. A sensor uses $2.0 \times 10^{-4} \text{ A}$ of current when it is operated by a 3.0-V battery. What is the resistance of the sensor circuit?
9. A lamp draws a current of 0.50 A when it is connected to a 120-V source.
 - a. What is the resistance of the lamp?
 - b. What is the power consumption of the lamp?
10. A 75-W lamp is connected to 125 V.
 - a. What is the current through the lamp?
 - b. What is the resistance of the lamp?
11. A resistor is added to the lamp in the previous problem to reduce the current to half of its original value.
 - a. What is the potential difference across the lamp?
 - b. How much resistance was added to the circuit?
 - c. How much power is now dissipated in the lamp?

QUICK DEMO

Alternating Current and Resonance





Estimated Time 15 minutes

Materials solar cell, amplifier, speaker, stroboscope

Procedure The following demonstration can show the beat production from constructive interference. Connect the solar cell to the

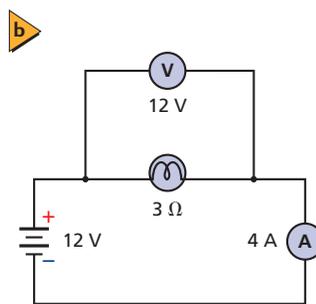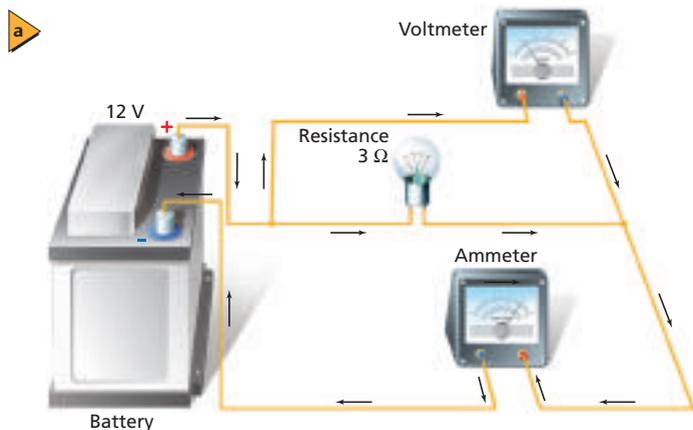amplifier and speaker. Expose the circuit to fluorescent lights. Students should be able to hear the 60 Hz hum. Turn the lights on and off, and ask students to listen to the difference. You can expand the demonstration by flashing a strobe light at 59 Hz or 61 Hz. Note the resulting beats. Refer to visual aids showing waves and constructive interference.



■ **Figure 22-7** A simple electric circuit is represented pictorially (a) and schematically (b).

An artist's drawing and a schematic of the same circuit are shown in **Figures 22-7a** and **22-7b**. Notice in both the drawing and the schematic that the electric charge is shown flowing out of the positive terminal of the battery. To draw schematic diagrams, use the problem-solving strategy below, and always set up a conventional current.

You learned that an ammeter measures current and a voltmeter measures potential differences. Each instrument has two terminals, usually labeled + and -. A voltmeter measures the potential difference across any component of a circuit. When connecting the voltmeter in a circuit, always connect the + terminal to the end of the circuit component that is closer to the positive terminal of the battery, and connect the - terminal to the other side of the component.

PROBLEM-SOLVING Strategies

Drawing Schematic Diagrams

Follow these steps when drawing schematic diagrams.

1. Draw the symbol for the battery or other source of electric energy, such as a generator, on the left side of the page. Put the positive terminal on top.
2. Draw a wire coming out of the positive terminal. When you reach a resistor or other device, draw the symbol for it.
3. If you reach a point where there are two current paths, such as at a voltmeter, draw a  in the diagram. Follow one path until the two current paths join again. Then draw the second path.
4. Follow the current path until you reach the negative terminal of the battery.
5. Check your work to make sure that you have included all parts and that there are complete paths for the current to follow.

MINI LAB

Current Affairs



Do you think that current diminishes as it passes through different elements in the circuit? As a scientist, you can test this question.

1. Draw a circuit that includes a power supply and two miniature lamps.
2. Draw the circuit again and include an ammeter to measure the current between the power supply and the lamps.
3. In a third diagram, show the ammeter at a position to measure the current between the lamps.

Analyze and Conclude

4. **Predict** if the current between the lamps will be more than, less than, or the same as the current before the lamps. Explain.
5. **Test** your prediction by building the circuits. **CAUTION: Wire is sharp and can cut skin.**

Using Models

A Car Battery Students can use the concept of resistance to model a partially drained battery. For example, a 12-V car battery might need to supply 200 A of current during engine cranking. If the resistance of the cranking motor is 0.060Ω , the required current is supplied: $12 \text{ V} / 0.060 \Omega = 200 \text{ A}$. A drained battery can be modeled as a $1\text{-}\Omega$ resistor. Combined with the resistance of the cranking motor, the new resistance is 1.060Ω . The current supplied would be about 11 A, not nearly enough to turn the engine. Point out that this model illustrates that measuring battery voltage with a meter that draws no current does not indicate whether the battery is able to do its job. For this reason, mechanics use a load test to evaluate a car's battery.

MINI LAB

Current Affairs

See page 37 of **FAST FILE Chapters 21–25 Resources** for the accompanying Mini Lab Worksheet.

CAUTION: Wire can scratch or cut skin.

Purpose to draw and build simple circuits and to investigate current at different points in a series circuit

Materials DC power supply (0 to 6 V), wires, miniature lamps and sockets (2), ammeter, protective eyewear

Expected Results Students should find that the current is the same at different points in a series circuit.

Analyze and Conclude

4. Students' predictions will vary.
5. Students should find that the current is the same at all points in the circuit.

Teacher F.Y.I.

CONTENT BACKGROUND

Energy Sources An important source of electric energy is realized by using a water turbine to convert the kinetic energy of falling water. The shaft of the turbine is used to turn a generator. The Hoover Dam has a total of 17 generators, each of which can generate up to 133 megawatts. The total capacity of the Hoover Dam hydropower plant is 2000 megawatts (2 gigawatts). Worldwide, hydropower plants produce about 24 percent of the world's electricity and supply more than a billion people with electric energy. There are more than 2000 hydropower plants operating in the United States, making hydropower the country's largest renewable energy source.

PRACTICE Problems

12. See Solutions Manual;
 $I = 4.80 \text{ A}$
13. See Solutions Manual;
 $R = 53 \ \Omega$
14. See Solutions Manual;
60.0 V for Practice Problem
12 and 4.5 V for Practice
Problem 13
15. See Solutions Manual
16. See Solutions Manual

3 ASSESS

Check for Understanding

Circuits Draw a complete circuit on the chalkboard in schematic form. Ask students whether the circuit is complete, to identify the symbols, to identify the source of energy, to identify the converter of energy, to indicate the direction of the current, whether Ohm's law applies, how power can be determined, and how energy can be determined. **L1 Visual-Spatial**

Extension

Batteries Ask students to explain rechargeable batteries from an energy point of view and to compare them to capacitors. A battery stores energy in chemical form and a capacitor stores energy in an electric field. As a battery discharges, current generated by the chemical reaction flows through the electrolyte. In a car's battery, for example, chemical reactions involving lead peroxide and sulfuric acid produce lead sulfate and water as the battery discharges. There is no chemical change within a capacitor as it is discharging. Instead, the electrostatic field resulting from the charge imbalance on the plates is being dissipated. **L2**

PRACTICE Problems

Additional Problems, Appendix B

12. Draw a circuit diagram to include a 60.0-V battery, an ammeter, and a resistance of $12.5 \ \Omega$ in series. Indicate the ammeter reading and the direction of the current.
13. Draw a series-circuit diagram showing a 4.5-V battery, a resistor, and an ammeter that reads 85 mA. Determine the resistance and label the resistor. Choose a direction for the conventional current and indicate the positive terminal of the battery.
14. Add a voltmeter to measure the potential difference across the resistors in problems 12 and 13 and repeat the problems.
15. Draw a circuit using a battery, a lamp, a potentiometer to adjust the lamp's brightness, and an on-off switch.
16. Repeat the previous problem, adding an ammeter and a voltmeter across the lamp.

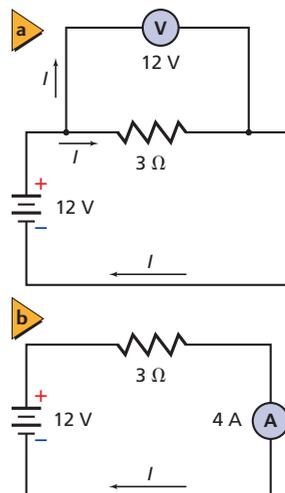


Figure 22-8 These schematics show a parallel (a) and a series circuit (b).

When a voltmeter is connected across another component, it is called a **parallel connection** because the circuit component and the voltmeter are aligned parallel to each other in the circuit, as diagrammed in **Figure 22-8a**. Any time the current has two or more paths to follow, the connection is labeled *parallel*. The potential difference across the voltmeter is equal to the potential difference across the circuit element. Always associate the words *voltage across* with a parallel connection.

An ammeter measures the current through a circuit component. The same current going through the component must go through the ammeter, so there can be only one current path. A connection with only one current path, called a **series connection**, is shown in **Figure 22-8b**. To add an ammeter to a circuit, the wire connected to the circuit component must be removed and connected to the ammeter instead. Then, another wire is connected from the second terminal of the ammeter to the circuit component. In a series connection, there can be only a single path through the connection. Always associate the words *current through* with a series connection.

22.1 Section Review

17. **Schematic** Draw a schematic diagram of a circuit that contains a battery and a lightbulb. Make sure the lightbulb will light in this circuit.
18. **Resistance** Joe states that because $R = V/I$, if he increases the voltage, the resistance will increase. Is Joe correct? Explain.
19. **Resistance** You want to measure the resistance of a long piece of wire. Show how you would construct a circuit with a battery, a voltmeter, an ammeter, and the wire to be tested to make the measurement. Specify what you would measure and how you would compute the resistance.
20. **Power** A circuit has $12 \ \Omega$ of resistance and is connected to a 12-V battery. Determine the change in power if the resistance decreases to $9.0 \ \Omega$.
21. **Energy** A circuit converts $2.2 \times 10^3 \text{ J}$ of energy when it is operated for 3.0 min. Determine the amount of energy it will convert when it is operated for 1 h.
22. **Critical Thinking** We say that power is “dissipated” in a resistor. To dissipate is to use, to waste, or to squander. What is “used” when charge flows through a resistor?

600 Chapter 22 Current Electricity

Physics online physicspp.com/self_check_quiz

22.1 Section Review

17. See Solutions Manual
18. No, resistance depends on the device. When V increases, so will I .
19. Measure the current through the wire and the potential difference across it. Divide the potential difference by the current to obtain the wire resistance.
20. 4.0 W increase
21. $44 \times 10^3 \text{ J}$
22. The potential energy of the charges decreases as they flow through the resistor. This decrease in potential energy is “used” to produce heat in the resistor.

22.2 Using Electric Energy

Section 22.2

Many familiar household appliances convert electric energy to some other form, such as light, kinetic energy, sound, or thermal energy. When you turn on one of these appliances, you complete a circuit and begin converting electric energy. In this section, you will learn to determine the rate of energy conversion and the amount that is converted.

Energy Transfer in Electric Circuits

Energy that is supplied to a circuit can be used in many different ways. A motor converts electric energy to mechanical energy, and a lamp changes electric energy into light. Unfortunately, not all of the energy delivered to a motor or a lamp ends up in a useful form. Lightbulbs, especially incandescent lightbulbs, become hot. Motors are often far too hot to touch. In each case, some of the electric energy is converted into thermal energy. You will now examine some devices that are designed to convert as much energy as possible into thermal energy.

Heating a resistor Current moving through a resistor causes it to heat up because flowing electrons bump into the atoms in the resistor. These collisions increase the atoms' kinetic energy and, thus, the temperature of the resistor. A space heater, a hot plate, and the heating element in a hair dryer all are designed to convert electric energy into thermal energy. These and other household appliances, such as those pictured in **Figure 22-9**, act like resistors when they are in a circuit. When charge, q , moves through a resistor, its potential difference is reduced by an amount, V . As you have learned, the energy change is represented by qV . In practical use, the rate at which energy is changed—the power, $P = E/t$ —is more important. Earlier, you learned that current is the rate at which charge flows, $I = q/t$, and that power dissipated in a resistor is represented by $P = IV$. For a resistor, $V = IR$. Thus, if you know I and R , you can substitute $V = IR$ into the equation for electric power to obtain the following.

$$\text{Power } P = I^2R$$

Power is equal to current squared times resistance.

Thus, the power dissipated in a resistor is proportional both to the square of the current passing through it and to the resistance. If you know V and R , but not I , you can substitute $I = V/R$ into $P = IV$ to obtain the following equation.

$$\text{Power } P = \frac{V^2}{R}$$

Power is equal to the voltage squared divided by the resistance.

Objectives

- **Explain** how electric energy is converted into thermal energy.
- **Explore** ways to deliver electric energy to consumers near and far.
- **Define** kilowatt-hour.

Vocabulary

- superconductor
- kilowatt-hour

1 FOCUS

Bellringer Activity

Rate of Change Submerge a $47\text{-}\Omega$, 10-W resistor in a small polystyrene cup half-filled with water. Use a thermometer to measure the water temperature. If time permits, run two trials, one with 10 volts applied and one with 20 volts applied. Note the rate of temperature increase. Ask students to announce the timed temperature readings, record the readings, and draw a graph on the chalkboard. **Visual-Spatial**

Tie to Prior Knowledge

Electric Energy Throughout this section students will connect the concepts associated with electric current and power to everyday uses of electric energy. They will also continue to explore the nature of the law of conservation of energy.

Figure 22-9 These appliances are designed to change electric energy into thermal energy.



Section 22.2 Using Electric Energy 601

Hutchings Photography

22.2 Resource MANAGER

FAST FILE Chapters 21–25 Resources

- Transparency 22-4 Master, p. 61
- Study Guide, pp. 47-48
- Section 22-2 Quiz, p. 50
- Physics Lab Worksheet, pp. 39-42

Teaching Transparency 22-4
Connecting Math to Physics

Technology

- TeacherWorks™ CD-ROM
- Interactive Chalkboard CD-ROM
- ExamView® Pro Testmaker CD-ROM
- physicspp.com
- physicspp.com/vocabulary_puzzlemaker

2 TEACH

▶ IN-CLASS Example

Question A water heater operates at 240 V, and the resistance of its heating element is 12 Ω . How much current does it demand, and how much heat energy will it produce in 30 minutes?



Answer $I = V/R$, $I = 240 \text{ V}/12 \Omega$,
 $I = 2.0 \times 10^1 \text{ A}$; $E = I^2 R t$, $E =$
 $(2.0 \times 10^1 \text{ A})^2 \times 12 \Omega \times 30 \text{ min} \times$
 $60 \text{ s}/1 \text{ min}$, $E = 8.6 \text{ MJ}$

Identifying Misconceptions

Thermostats Some students might think that a chilly room will heat faster by setting the thermostat higher and that a hot room will cool faster by setting the thermostat lower. In fact, a thermostat is an on-off switch and does not operate like the accelerator in a vehicle. For example, moving the thermostat to 75°F in a 65°F room will not make the temperature rise to 70°F more quickly than it would have if the thermostat had simply been set at 70°F.

Critical Thinking

Pollution Electric utility companies often tout the cleanliness of electric energy. Ask students why this is misleading. **Using electric energy is generally a nonpolluting process. However, producing electric energy is generally a polluting process. All forms of energy production involve trade-offs. Even “green” technologies such as wind and solar power have drawbacks: While these methods do not release chemical pollutants into the environment, they do create noise and cause problems for wildlife. Furthermore, the batteries that store the generated power can themselves be a source of pollution. L2**

The power is the rate at which energy is converted from one form to another. Energy is changed from electric to thermal energy, and the temperature of the resistor rises. If the resistor is an immersion heater or burner on an electric stovetop, for example, heat flows into cold water fast enough to bring the water to the boiling point in a few minutes.

If power continues to be dissipated at a uniform rate, then after time t , the energy converted to thermal energy will be $E = Pt$. Because $P = I^2 R$ and $P = V^2/R$, the total energy to be converted to thermal energy can be written in the following ways.

$$E = Pt$$

Thermal Energy $E = I^2 R t$

$$E = \left(\frac{V^2}{R}\right)t$$

Thermal energy is equal to the power dissipated multiplied by the time. It is also equal to the current squared multiplied by resistance and time as well as the voltage squared divided by resistance multiplied by time.

▶ EXAMPLE Problem 3

Electric Heat A heater has a resistance of 10.0 Ω . It operates on 120.0 V.

- What is the power dissipated by the heater?
- What thermal energy is supplied by the heater in 10.0 s?


1 Analyze and Sketch the Problem

- Sketch the situation.
- Label the known circuit components, which are a 120.0-V potential difference source and a 10.0- Ω resistor.

Known: $R = 10.0 \Omega$ **Unknown:** $P = ?$

$$V = 120.0 \text{ V} \quad E = ?$$

$$t = 10.0 \text{ s}$$

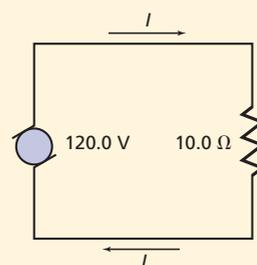

2 Solve for the Unknown

- Because R and V are known, use $P = V^2/R$.

$$P = \frac{(120.0 \text{ V})^2}{10.0 \Omega}$$

$$= 1.44 \text{ kW}$$

Substitute $V = 120.0 \text{ V}$, $R = 10.0 \Omega$

- Solve for the energy.

$$E = Pt$$

$$= (1.44 \text{ kW})(10.0 \text{ s})$$

$$= 14.4 \text{ kJ}$$

Substitute $P = 1.44 \text{ kW}$, $t = 10.0 \text{ s}$

Math Handbook

Exponents
page 839

3 Evaluate the Answer

- Are the units correct?** Power is measured in watts, and energy is measured in joules.
- Are the magnitudes realistic?** For power, $10^2 \times 10^2 \times 10^{-1} = 10^3$, so kilowatts is reasonable. For energy, $10^3 \times 10^1 = 10^4$, so an order of magnitude of 10,000 joules is reasonable.

CHALLENGE

Activity

Capacitance Use a 1000- $\mu\text{F}/25\text{-V}$ electrolytic capacitor, a 12-V DC power supply, and a 12-V lamp to demonstrate charge/energy storage. **CAUTION: Observe polarity.** Ask students to explain how there is sufficient current in this circuit to light the lamp when the capacitor has a DC resistance in the range of $10^6 \Omega$. **CAUTION: Do not attempt to measure the resistance of the capacitor when it is charged.** Short the capacitor leads for a minute or so before making such a measurement. **L3 Visual-Spatial**

PRACTICE Problems

Additional Problems, Appendix B

23. A 15- Ω electric heater operates on a 120-V outlet.
- What is the current through the heater?
 - How much energy is used by the heater in 30.0 s?
 - How much thermal energy is liberated in this time?
24. A 39- Ω resistor is connected across a 45-V battery.
- What is the current in the circuit?
 - How much energy is used by the resistor in 5.0 min?
25. A 100.0-W lightbulb is 22 percent efficient. This means that 22 percent of the electric energy is converted to light energy.
- How many joules does the lightbulb convert into light each minute it is in operation?
 - How many joules of thermal energy does the lightbulb produce each minute?
26. The resistance of an electric stove element at operating temperature is 11 Ω .
- If 220 V are applied across it, what is the current through the stove element?
 - How much energy does the element convert to thermal energy in 30.0 s?
 - The element is used to heat a kettle containing 1.20 kg of water. Assume that 65 percent of the heat is absorbed by the water. What is the water's increase in temperature during the 30.0 s?
27. A 120-V water heater takes 2.2 h to heat a given volume of water to a certain temperature. How long would a 240-V unit operating with the same current take to accomplish the same task?

Superconductors A **superconductor** is a material with zero resistance. There is no restriction of current in superconductors, so there is no potential difference, V , across them. Because the power that is dissipated in a conductor is given by the product IV , a superconductor can conduct electricity without loss of energy. At present, almost all superconductors must be kept at temperatures below 100 K. The practical uses of superconductors include MRI magnets and in synchrotrons, which use huge amounts of current and can be kept at temperatures close to 0 K.

Transmission of Electric Energy

Hydroelectric facilities, such as the one at Itaipu Dam, shown in **Figure 22-10**, are capable of producing a great deal of energy. This hydroelectric energy often must be transmitted over long distances to reach homes and industries. How can the transmission occur with as little loss to thermal energy as possible?

Thermal energy is produced at a rate represented by $P = I^2R$. Electrical engineers call this unwanted thermal energy the joule heating loss, or I^2R loss. To reduce this loss, either the current, I , or the resistance, R , must be reduced.

All wires have some resistance, even though their resistance is small. The large wire used to carry electric current into a home has a resistance of 0.20 Ω for 1 km.

■ **Figure 22-10** In the year 2000, energy produced by Itaipu Dam met 24 percent of Brazil's electric energy needs and 95 percent of Paraguay's.



Section 22.2 Using Electric Energy 603
Hans-Jurgen Burkard/Peter Arnold, Inc.

PRACTICE Problems

23. a. 8.0 A b. 2.9×10^4 J
c. 2.9×10^4 J
24. a. 1.2 A b. 1.6×10^4 J
25. a. 1.3×10^3 J b. 4.7×10^3 J
26. a. 2.0×10^1 A b. 1.3×10^5 J
c. 17°C
27. doubling the voltage will divide the time by 2;
 $t = 1.1$ h

QUICK DEMO

Energy Storage

Estimated Time 10 minutes

Materials 1- μ F capacitor, 9-V battery, digital multimeter (DMM), 1-M Ω resistor

Procedure Use this demonstration to show energy storage in a capacitor. Set up the circuit and time the discharge of the capacitor. Be sure to observe capacitor polarity. A typical DMM has a resistance of 10 M Ω , and the time required to discharge the capacitor is approximately $5RC = 5(10 \text{ M}\Omega)(1 \mu\text{F}) = 50$ s. Repeat the demonstration with a 1-M Ω resistor in parallel with the meter leads, which will show an order-of-magnitude decrease in the discharge time.

Discussion

Question Why are high-voltage lines located on high towers?

Answer Locating high-voltage lines on towers is done for safety reasons. Voltages of hundreds of thousands of volts are extremely dangerous. The insulation materials that would be required to locate the cables near ground or underground would be impractical. The high towers allow air to serve as the major insulator. **L2**

PHYSICS PROJECT

Activity

Superconductors Have students prepare a report explaining the reasons that some materials begin to superconduct at very low temperatures. Students should discover that conductors hold their electrons loosely; however, moving electrons lose energy in the form of heat as they collide with atoms in the conductor. Electrons traveling in superconductors experience less energy loss because they readily travel in pairs. While this advantageous pairing can take place at high temperatures, in superconductors low temperatures make it easier for electrons to pair up and move quickly between atoms with essentially zero energy loss. **L2 Linguistic**

Using Figure 22-11

Ask students to suppose you have a digital watt-hour meter. Also suppose that there is no current at this moment (everything in the building is turned off). Ask them will the meter reading go to zero? **No, the last reading will hold because the meter is indicating the total energy used.** **L2**

Concept Development

Stereos and Power Some people want sound systems that are very powerful in their vehicles. This is difficult to achieve with a 12-V system, given that speakers are usually 4.0Ω . In such a system, the power delivered to one speaker is limited to 36 W (V^2/R). One solution is to use a bridge-type amplifier, which effectively doubles the speaker voltage (for four times the power).

Reinforcement

Energy Use Display an immersion-type water heater and the heating element from an electric water heater. Ask students what differences exist between the two devices. **Items that could be mentioned in the ensuing discussion include size, cost, resistance, voltage rating, and reliability.**

L2 Logical-Mathematical



Figure 22-11 Watt-hour meters measure the amount of electric energy used by a consumer (a). Meter readings then are used in calculating the cost of energy (b).

Suppose that a farmhouse were connected directly to a power plant 3.5 km away. The resistance in the wires needed to carry a current in a circuit to the home and back to the plant is represented by the following equation: $R = 2(3.5 \text{ km})(0.20 \Omega/\text{km}) = 1.4 \Omega$. An electric stove might cause a 41-A current through the wires. The power dissipated in the wires is represented by the following relationships: $P = I^2R = (41 \text{ A})^2 (1.4 \Omega) = 2400 \text{ W}$.

All of this power is converted to thermal energy and, therefore, is wasted. This loss could be minimized by reducing the resistance. Cables of high conductivity and large diameter (and therefore low resistance) are available, but such cables are expensive and heavy. Because the loss of energy is also proportional to the square of the current in the conductors, it is even more important to keep the current in the transmission lines low.


How can the current in the transmission lines be kept low? The electric energy per second (power) transferred over a long-distance transmission line is determined by the relationship $P = IV$. The current is reduced without the power being reduced by an increase in the voltage. Some long-distance lines use voltages of more than 500,000 V. The resulting lower current reduces the I^2R loss in the lines by keeping the I^2 factor low. Long-distance transmission lines always operate at voltages much higher than household voltages in order to reduce I^2R loss. The output voltage from the generating plant is reduced upon arrival at electric substations to 2400 V, and again to 240 V or 120 V before being used in homes.

The Kilowatt-Hour

While electric companies often are called power companies, they actually provide energy rather than power. Power is the rate at which energy is delivered. When consumers pay their home electric bills, an example of which is shown in **Figure 22-11**, they pay for electric energy, not power.

The amount of electric energy used by a device is its rate of energy consumption, in joules per second (W) times the number of seconds that the device is operated. Joules per second times seconds, (J/s)s, equals the total amount of joules of energy. The joule, also defined as a watt-second, is a relatively small amount of energy, too small for commercial sales use. For this reason, electric companies measure energy sales in a unit of a

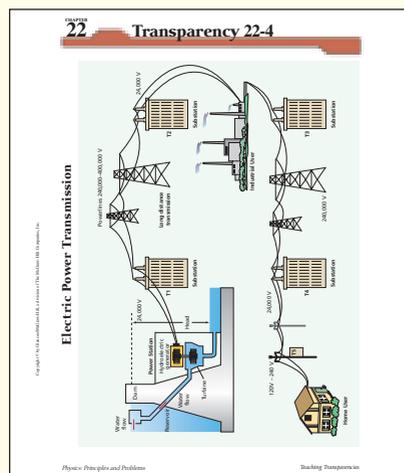
Page 61, **FAST FILE**
Chapters 21–25 Resources



CHALLENGE PROBLEM

Use the figure to the right to help you answer the questions below.

- Initially, the capacitor is uncharged. Switch 1 is closed, and Switch 2 remains open. What is the voltage across the capacitor?
- Switch 1 is now opened, and Switch 2 remains open. What is the voltage across the capacitor? Why?
- Next, Switch 2 is closed, while Switch 1 remains open. What is the voltage across the capacitor and the current through the resistor immediately after Switch 2 is closed?
- As time goes on, what happens to the voltage across the capacitor and the current through the resistor?

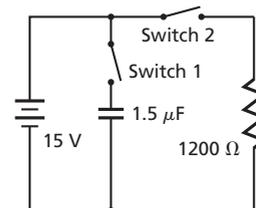

604 Chapter 22 Current Electricity

(t)Bischel Studios, (b)Hutchings Photography

CHALLENGE PROBLEM

- 15 V
- It remains 15 V because there is no path for the charge to be removed.
- 15 V and 13 mA
- The capacitor voltage remains at 15 V because there is no path to discharge the capacitor; the current remains at

13 mA because the battery voltage is constant at 15 V. However, if the battery and capacitor were real components instead of ideal circuit components, the capacitor voltage would eventually become zero due to leakage and the current would eventually become zero due to battery depletion.

large number of joules called a kilowatt-hour, kWh. A **kilowatt-hour** is equal to 1000 watts delivered continuously for 3600 s (1 h), or 3.6×10^6 J. Not many household devices other than hot-water heaters, stoves, clothes dryers, microwave ovens, heaters, and hair dryers require more than 1000 W of power. Ten 100-W lightbulbs operating all at once use only 1 kWh of energy when they are left on for one full hour.

PRACTICE Problems

Additional Problems, Appendix B

28. An electric space heater draws 15.0 A from a 120-V source. It is operated, on the average, for 5.0 h each day.
 - a. How much power does the heater use?
 - b. How much energy in kWh does it consume in 30 days?
 - c. At \$0.12 per kWh, how much does it cost to operate the heater for 30 days?
29. A digital clock has a resistance of 12,000 Ω and is plugged into a 115-V outlet.
 - a. How much current does it draw?
 - b. How much power does it use?
 - c. If the owner of the clock pays \$0.12 per kWh, how much does it cost to operate the clock for 30 days?
30. An automotive battery can deliver 55 A at 12 V for 1.0 h and requires 1.3 times as much energy for recharge due to its less-than-perfect efficiency. How long will it take to charge the battery using a current of 7.5 A? Assume that the charging voltage is the same as the discharging voltage.
31. Rework the previous problem by assuming that the battery requires the application of 14 V when it is recharging.

You have learned several ways in which power companies solve the problems involved in transmitting electric current over great distances. You also have learned how power companies calculate electric bills and how to predict the cost of running various appliances in the home. The distribution of electric energy to all corners of Earth is one of the greatest engineering feats of the twentieth century.

22.2 Section Review

32. **Energy** A car engine drives a generator, which produces and stores electric charge in the car's battery. The headlamps use the electric charge stored in the car battery. List the forms of energy in these three operations.
33. **Resistance** A hair dryer operating from 120 V has two settings, hot and warm. In which setting is the resistance likely to be smaller? Why?
34. **Power** Determine the power change in a circuit if the applied voltage is decreased by one-half.
35. **Efficiency** Evaluate the impact of research to improve power transmission lines on society and the environment.
36. **Voltage** Why would an electric range and an electric hot-water heater be connected to a 240-V circuit rather than a 120-V circuit?
37. **Critical Thinking** When demand for electric power is high, power companies sometimes reduce the voltage, thereby producing a "brown-out." What is being saved?

Physics online physicspp.com/self_check_quiz

Section 22.2 Using Electric Energy 605

22.2 Section Review

32. Mechanical energy from the engine converted to electric energy in the generator; electric energy stored as chemical energy in the battery; chemical energy converted to electric energy in the battery; electric energy converted to light and thermal energy in the headlamps.

33. Hot draws more power, $P = IV$, so the fixed voltage current is larger. Because $I = V/R$ the resistance is smaller.
34. It will decrease to one-fourth of the original value.
35. Some potential benefits: lower cost of electricity, if less power were lost during transmission, less coal and other power-producing resources

- would be used, which would improve the quality of our environment.
36. For the same power, at twice the voltage, the current would be halved. The I^2R loss in the circuit wiring would be dramatically reduced because it is proportional to the square of the current.
37. Power, not energy; most devices will have to run longer.

PRACTICE Problems

28. a. 1.8 kW b. 270 kWh
c. \$32.40
29. a. 9.6×10^{-3} A b. 1.1 W
c. \$0.10
30. 9.5 h
31. 8.2 h

3 ASSESS

Check for Understanding

Consumption and Cost To help students understand energy consumption and cost, ask them to compare the cost of operating various household appliances by explaining the relationships among power, current draw, and the cost of operating 1000-W, 250-W and 50-W appliances at household voltages. Assuming all other variables are equal and only power changes, as the power increases, the current draw and operating cost would increase. **L2**

Extension

Future Energy Production

Assign students a research project relating to the possible future use of nuclear fusion for generating electricity. Students should compare fission, fusion, and combustion processes. **L2 Linguistic**

Voltage, Current, and Resistance

In this chapter, you studied the relationships between voltage, current, and resistance in simple circuits. Voltage is the potential difference that pushes current through a circuit, while resistance determines how much current will flow if a potential difference exists. In this activity, you will collect data and make graphs in order to investigate the mathematical relationships between voltage and current and between resistance and current.

QUESTION

What are the relationships between voltage and current and resistance and current?

Objectives

- **Measure** current in SI.
- **Describe** the relationship between the resistance of a circuit and the total current flowing through a circuit.
- **Describe** the relationship between voltage and the total current flowing through a circuit.
- **Make and use graphs** to show the relationships between current and resistance and between current and voltage.

Safety Precautions



- **CAUTION: Resistors and circuits may become hot.**
- **CAUTION: Wires are sharp and can cut skin.**

Materials

- four 1.5-V D batteries
- four D-battery holders
- one 10-k Ω resistor
- one 500- μ A ammeter
- five wires with alligator clips
- one 20-k Ω resistor
- one 30-k Ω resistor
- one 40-k Ω resistor

Procedure

Part A

1. Place the D battery in the D-battery holder.
2. Create a circuit containing the D battery, 10-k Ω resistor, and 500- μ A ammeter.
3. Record the values for resistance and current in Data Table 1. For resistance, use the value of the resistor. For current, read and record the value given by the ammeter.
4. Replace the 10-k Ω resistor with a 20-k Ω resistor.
5. Record the resistance and the current in Data Table 1.
6. Repeat steps 4–5, but replace the 20-k Ω resistor with a 30-k Ω resistor.
7. Repeat steps 4–5, but replace the 30-k Ω resistor with a 40-k Ω resistor.

Part B

8. Recreate the circuit that you made in step 2. Verify the current in the circuit and record the values for voltage and current in Data Table 2.
9. Add a second 1.5-V D battery to the setup and record the values for voltage and current in Data Table 2. When you are using more than one battery, record the sum of the batteries' voltages as the voltage in Data Table 2.
10. Repeat step 9 with three 1.5-V D batteries.
11. Repeat step 9 with four 1.5-V D batteries.

Time Allotment

This lab will probably take two 50-min periods to set up the circuits and collect and analyze the data. As an alternative, collect the data over one 50-min period and assign the analysis as work for outside of class.

Process Skills describe, measure in SI, make and use graphs

Safety Precautions Circuits may become hot. Always wear proper eye protection and clothing protection in the lab. Wire can scratch or cut skin.



Alternative Materials Power sources, ammeters, and resistors of various sizes can be used. Equal resistors in series will have the same effect as using larger resistors; that is covered in Chapter 23.

Teaching Strategies

- If you vary the materials, it is important to test your setup to make sure that the current is not too strong or too weak for the circuit.
- If you can get the students to develop the relationship $I = k/R$ and $V = kI$ (where k is a constant), they should be able to develop the relationship $V = IR$.

Analyze

1.

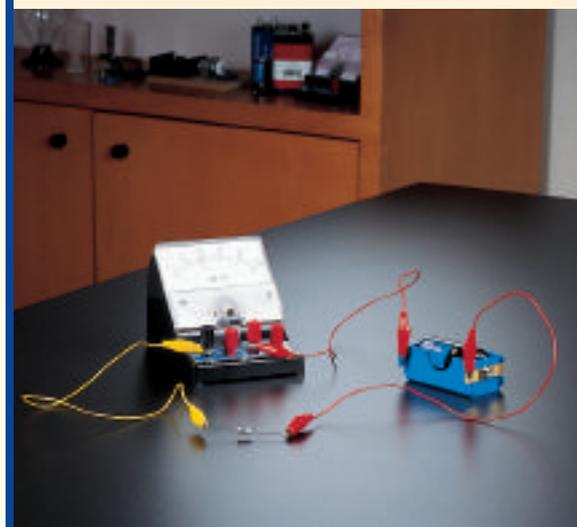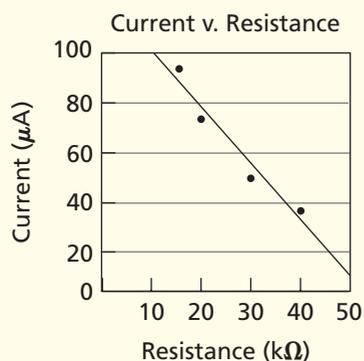

606
Horizons Companies

Sample Data

Data Table 1

Voltage (V)	Resistance (k Ω)	Current (μ A)
1.5	16	94
1.5	20	75
1.5	30	50
1.5	40	38

Data Table 2

Voltage (V)	Resistance (k Ω)	Current (μ A)
1.5	10	160
3.0	10	300
4.5	10	420
6.0	10	510

Data Table 1		
Voltage (V)	Resistance (k Ω)	Current (μ A)
1.5		
1.5		
1.5		
1.5		

Data Table 2		
Voltage (V)	Resistance (k Ω)	Current (μ A)
	10	
	10	
	10	
	10	

Analyze

- Make and Use Graphs** Graph the current versus the resistance. Place resistance on the x -axis and current on the y -axis.
- Make and Use Graphs** Graph the current versus the voltage. Place voltage on the x -axis and current on the y -axis.
- Error Analysis** Other than the values of the resistors, what factors could have affected the current in Part A? How might the effect of these factors be reduced?
- Error Analysis** Other than the added batteries, what factors could have affected the current in Part B? How might the effect of these factors be reduced?

Conclude and Apply

- Looking at the first graph that you made, describe the relationship between resistance and current?
- Why do you suppose this relationship between resistance and current exists?
- Looking at the second graph that you made, how would you describe the relationship between voltage and current?
- Why do you suppose this relationship between voltage and current exists?

Going Further


- What would be the current in a circuit with a voltage of 3.0 V and a resistance of 20 k Ω ? How did you determine this?
- Could you derive a formula from your lab data to explain the relationship among voltage, current, and resistance? *Hint: Look at the graph of current versus voltage. Assume it is a straight line that goes through the origin.*
- How well does your data match this formula? Explain.

Real-World Physics

- Identify some common appliances that use 240 V rather than 120 V.
- Why do the appliances that you identified require 240 V? What would be the consequences for running such an appliance on a 120-V circuit?

Physics online

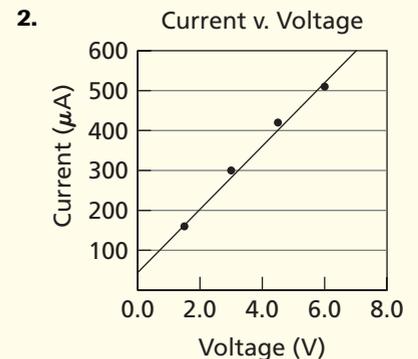To find out more about current electricity, visit the Web site: physicspp.com



- In real batteries, terminal voltage does decrease over time. Any change in voltage will affect current.
- Again, any change in the terminal voltage of the batteries will affect the current.

Conclude and Apply

- There is an inverse relationship between resistance and current. As resistance increases, current decreases, and vice versa.
- This relationship exists because current is inversely proportional to resistance (I or $1/R$).
- There is a linear relationship between voltage and current. As voltage increases, current increases.
- This relationship exists because voltage increases the potential energy of the charges.

Going Further

- The current would be around 160 μ A. Doubling the voltage will compensate for the doubling of the resistance.
- $V = IR$
- The data should match rather well but may become further off as current increases.

Real-World Physics

- Answers include electric ranges, hot water heaters, dryers, and refrigerators.
- Since $P = IV$ and P stays the same, the current will go up if voltage drops. As a result, much more energy will be dissipated as heat.

ALTERNATIVE INQUIRY LAB

To Make this Lab an Inquiry Lab: Ask the students to design an experiment to find the relationship between current, voltage, and resistance. Emphasize that they should only change one variable at a time and be sure to teach them what instruments measure each of these quantities. Make students aware of the possibility of burning or shorting the circuit.

Hybrid Cars

Background

There are two basic types of hybrid cars, parallel hybrids and series hybrids. The student text describes a simple parallel hybrid, which is the more common type as of 2003. In a parallel hybrid, both the gas engine and electric motor are linked directly to the transmission; however, in a series hybrid, the gas engine is linked directly to a generator. The generator supplies energy to the batteries or to an electric motor, which then moves the car. Series hybrids do not idle; the gas engine shuts down entirely when the car is stopped.

Teaching Strategies

- Today, more than half the oil the United States uses is imported. Have students write a paragraph analyzing the advantages and disadvantages of importing oil. For example, buying oil from other countries provides those countries with needed income and stability; however, guaranteeing the supply might be expensive or impossible, and using fossil fuels adds to pollution.
- Discuss the potential costs and benefits of other alternative sources of energy, such as hydrogen fuel cells. (Note: splitting water into hydrogen and oxygen requires energy. Energy is not created from “nothing.” There is an energy cost to creating any source of power.)


Activity

Attitude Change Have students interview people such as parents or grandparents and ask them if they have changed their attitudes toward fossil fuels over the course of their lifetimes. Have students ask the people interviewed if they would consider a hybrid car for their next vehicle, and why they would consider it: fuel efficiency? performance? economy? image?

Meet the hybrid car. It is fuel-efficient, comfortable, safe, quiet, clean, and it accelerates well. Hybrid sales are growing and are expected to exceed 200,000 vehicles in 2005.

Why are they called hybrids? A vehicle is called a hybrid if it uses two or more sources of energy. For example, diesel-electric locomotives are hybrids. But the term *hybrid vehicle* usually refers to a car that uses gas and electricity.

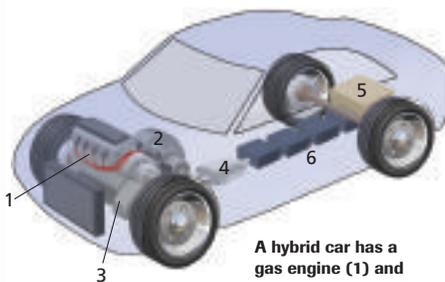
Conventional cars have large engines that enable them to accelerate quickly and to drive up steep hills. But the engine's size makes it inefficient. In a hybrid, a lighter, more efficient gas engine meets most driving needs. When extra energy is needed, it is supplied by electricity from rechargeable batteries.



A hybrid car has a gas engine (1) and an electric motor (2).

How do hybrids work? The illustration above shows one type of hybrid, called a parallel hybrid. The small internal combustion engine (1) powers the car during most driving situations. The gas engine and electric motor (2) are connected to the wheels by the same transmission (3). Computerized electronics (4) decide when to use the electric motor, when to use the engine, and when to use both.

This type of hybrid has no external power source besides the gas in the fuel tank (5). Unlike an electric car, you don't need to plug the hybrid into an electric outlet to recharge the batteries (6). Rather, the batteries are recharged by a process called regenerative braking, as shown in the schematic diagram. In conventional vehicles, the brakes apply friction to the wheels, converting a vehicle's kinetic energy into heat. However, a hybrid's electric motor

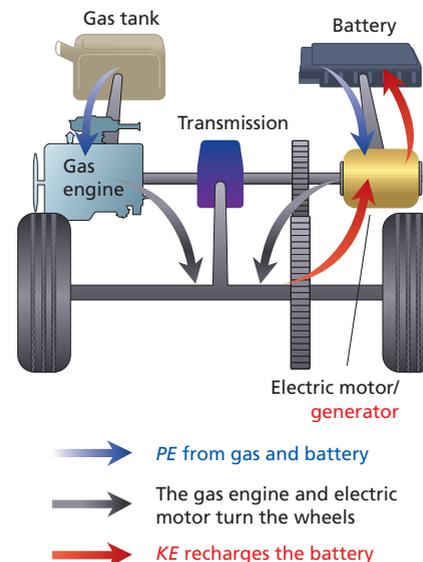

In regenerative braking, energy from the moving car recharges the batteries.

can act as a generator. When the electric motor slows the car, kinetic energy is converted to electric energy, which then recharges the batteries.

Can hybrids benefit society? Hybrid cars improve gas mileage and reduce tailpipe emissions. Improved gas mileage saves on the cost of operating the car. Tailpipe emissions include carbon dioxide and carbon monoxide, as well as various hydrocarbons and nitrogen oxides. These emissions can contribute to certain problems, such as smog. Because hybrids improve gas mileage and reduce tailpipe emissions, many people feel that these cars are one viable way to help protect air quality and conserve fuel resources.

Going Further

1. **Analyze and Conclude** What is regenerative braking?
2. **Predict** Will increased sales of hybrids benefit society? Support your answer.

Going Further

1. **Regenerative braking is the process by which a hybrid converts kinetic energy to electric energy as the brakes are applied.**
2. **Accept all reasonable answers. Two stated benefits are lowered tailpipe emissions and better fuel economy.**

22.1 Current and Circuits

Vocabulary

- electric current (p. 592)
- conventional current (p. 592)
- battery (p. 592)
- electric circuit (p. 592)
- ampere (p. 593)
- resistance (p. 595)
- resistor (p. 596)
- parallel connection (p. 600)
- series connection (p. 600)

Key Concepts

- Conventional current is defined as current in the direction in which a positive charge would move.
- Generators convert mechanical energy to electric energy.
- A circuit converts electric energy to heat, light, or some other useful output.
- As charge moves through a circuit, resistors cause a drop in potential energy.
- An ampere is equal to one coulomb per second (1 C/s).
- Power can be found by multiplying voltage times current.

$$P = IV$$

- The resistance of a device is given by the ratio of the device's voltage to its current.

$$R = \frac{V}{I}$$

- Ohm's law states that the ratio of potential difference to current is a constant for a given conductor. Any resistance that does not change with temperature, voltage, or the direction of charge flow obeys Ohm's law.
- Circuit current can be controlled by changing voltage, resistance, or both.

22.2 Using Electric Energy

Vocabulary

- superconductor (p. 603)
- kilowatt-hour (p. 605)

Key Concepts

- The power in a circuit is equal to the square of the current times the resistance, or to the voltage squared divided by the resistance.

$$P = I^2R \text{ or } P = \frac{V^2}{R}$$

- If power is dissipated at a uniform rate, the thermal energy converted equals power multiplied by time. Power also can be represented by I^2R and V^2/R to give the last two equations.

$$\begin{aligned} E &= Pt \\ &= I^2Rt \\ &= \left(\frac{V^2}{R}\right)t \end{aligned}$$

- Superconductors are materials with zero resistance. At present, the practical uses of superconductors are limited.
- Unwanted thermal energy produced in the transmission of electric energy is called the joule heating loss, or I^2R loss. The best way to minimize the joule heating loss is to keep the current in the transmission wires low. Transmitting at higher voltages enables current to be reduced without power being reduced.
- The kilowatt-hour, kWh, is an energy unit. It is equal to 3.6×10^6 J.

Key Concepts

Summary statements can be used by students to review the major concepts of the chapter.



Visit physicspp.com

[/self_check_quiz](#)

[/vocabulary_puzzlemaker](#)

[/chapter_test](#)

[/standardized_test](#)

VOCABULARY
PuzzleMaker

PHYSICS

ONLINE

For additional help with vocabulary, have students access the Vocabulary PuzzleMaker online.

physicspp.com/vocabulary_puzzlemaker

Concept Mapping

38. See Solutions Manual.

Mastering Concepts

39. $1A = 1 C/1 s$

40. The positive voltmeter lead connects to the left-hand motor lead, and the negative voltmeter lead connects to the right-hand motor lead.

41. Break the circuit between the battery and the motor. Then connect the positive ammeter lead to the positive side of the break (the side connected to the positive battery terminal) and the negative ammeter lead to the negative side (the side nearest the motor).

42. from left to right through the motor

43. a. 4
b. 1
c. 2
d. 3

44. a. electric energy to heat and light
b. electric energy to heat and kinetic energy
c. electric energy to light and sound

45. A larger-diameter wire has a smaller resistance because there are more electrons to carry the charge.


46. a. See Solutions Manual.
b. The ammeter must be connected in series.
c. The voltmeter must be connected in parallel.

47. The low resistance of the cold filament allows a high current initially and a greater change in temperature, subjecting the filament to greater stress.

48. The short circuit produces a high current, which causes more electrons to collide with the atoms of the wire. This raises the atoms' kinetic energy and the temperature of the wire.

Concept Mapping

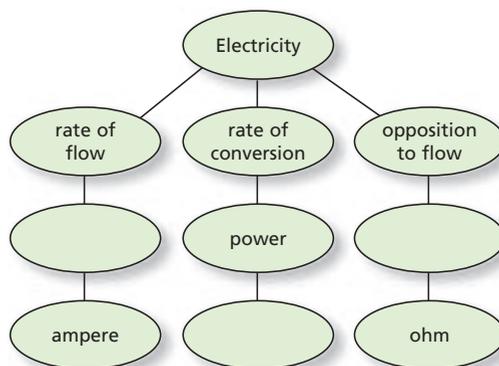38. Complete the concept map using the following terms: *watt, current, resistance*.



Mastering Concepts

39. Define the unit of electric current in terms of fundamental MKS units. (22.1)

40. How should a voltmeter be connected in Figure 22-12 to measure the motor's voltage? (22.1)

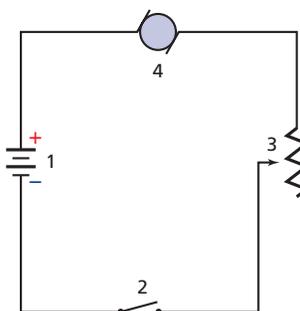


Figure 22-12

41. How should an ammeter be connected in Figure 22-12 to measure the motor's current? (22.1)

42. What is the direction of the conventional motor current in Figure 22-12? (22.1)

43. Refer to Figure 22-12 to answer the following questions. (22.1)

- Which device converts electric energy to mechanical energy?
- Which device converts chemical energy to electric energy?
- Which device turns the circuit on and off?
- Which device provides a way to adjust speed?

610 Chapter 22 Current Electricity For more problems, go to Additional Problems, Appendix B.

44. Describe the energy conversions that occur in each of the following devices. (22.1)

- an incandescent lightbulb
- a clothes dryer
- a digital clock radio

45. Which wire conducts electricity with the least resistance: one with a large cross-sectional diameter or one with a small cross-sectional diameter? (22.1)

46. A simple circuit consists of a resistor, a battery, and connecting wires. (22.1)

- Draw a circuit schematic of this simple circuit.
- How must an ammeter be connected in a circuit for the current to be correctly read?
- How must a voltmeter be connected to a resistor for the potential difference across it to be read?

47. Why do lightbulbs burn out more frequently just as they are switched on rather than while they are operating? (22.2)

48. If a battery is short-circuited by a heavy copper wire being connected from one terminal to the other, the temperature of the copper wire rises. Why does this happen? (22.2)

49. What electric quantities must be kept small to transmit electric energy economically over long distances? (22.2)

50. Define the unit of power in terms of fundamental MKS units. (22.2)

Applying Concepts

51. **Batteries** When a battery is connected to a complete circuit, charges flow in the circuit almost instantaneously. Explain.

52. Explain why a cow experiences a mild shock when it touches an electric fence.

53. **Power Lines** Why can birds perch on high-voltage lines without being injured?

54. Describe two ways to increase the current in a circuit.

55. **Lightbulbs** Two lightbulbs work on a 120-V circuit. One is 50 W and the other is 100 W. Which bulb has a higher resistance? Explain.

56. If the voltage across a circuit is kept constant and the resistance is doubled, what effect does this have on the circuit's current?

57. What is the effect on the current in a circuit if both the voltage and the resistance are doubled? Explain.

49. The resistance of the wire and the current in the wire

$$50. W = \frac{C \cdot J}{s \cdot C} = \frac{J}{s} = \frac{\text{kg} \cdot \frac{\text{m}^2}{\text{s}^2}}{\text{s}} = \frac{\text{kg} \cdot \text{m}^2}{\text{s}^3}$$

Applying Concepts

51. A potential difference is felt over the entire circuit as soon as the battery is connected to the circuit. The potential difference causes the charges to begin to flow. Note: The charges flow slowly compared to the change in potential difference.

52. By touching the fence and the ground, the cow encounters a difference in potential and conducts current, thus receiving a shock.

53. No potential difference exists along the wires, so no current flows through the bird's body.

54. Either increase the voltage or decrease the resistance.

58. **Ohm's Law** Sue finds a device that looks like a resistor. When she connects it to a 1.5-V battery, she measures only 45×10^{-6} A, but when she uses a 3.0-V battery, she measures 25×10^{-3} A. Does the device obey Ohm's law?
59. If the ammeter in Figure 22-4a on page 596 were moved to the bottom of the diagram, would the ammeter have the same reading? Explain.
60. Two wires can be placed across the terminals of a 6.0-V battery. One has a high resistance, and the other has a low resistance. Which wire will produce thermal energy at a faster rate? Why?

Mastering Problems

22.1 Current and Circuits

61. A motor is connected to a 12-V battery, as shown in Figure 22-13.
- How much power is delivered to the motor?
 - How much energy is converted if the motor runs for 15 min?

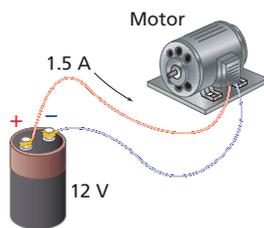


Figure 22-13

62. Refer to Figure 22-14 to answer the following questions.
- What should the ammeter reading be?
 - What should the voltmeter reading be?
 - How much power is delivered to the resistor?
 - How much energy is delivered to the resistor per hour?

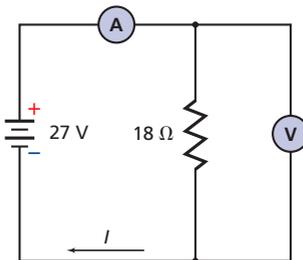


Figure 22-14

63. Refer to Figure 22-15 to answer the following questions.
- What should the ammeter reading be?
 - What should the voltmeter reading be?
 - How much power is delivered to the resistor?
 - How much energy is delivered to the resistor per hour?

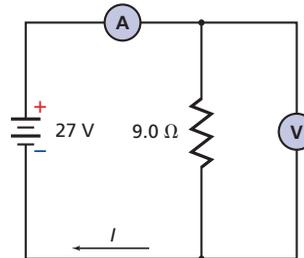


Figure 22-15

64. Refer to Figure 22-16 to answer the following questions.
- What should the ammeter reading be?
 - What should the voltmeter reading be?
 - How much power is delivered to the resistor?
 - How much energy is delivered to the resistor per hour?

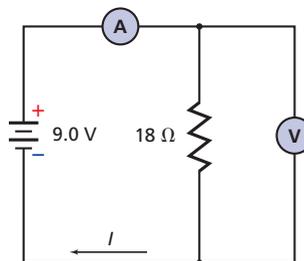


Figure 22-16

65. **Toasters** The current through a toaster that is connected to a 120-V source is 8.0 A. What power is dissipated by the toaster?
66. **Lightbulbs** A current of 1.2 A is measured through a lightbulb when it is connected across a 120-V source. What power is dissipated by the bulb?
67. A lamp draws 0.50 A from a 120-V generator.
- How much power is delivered?
 - How much energy is converted in 5.0 min?
68. A 12-V automobile battery is connected to an electric starter motor. The current through the motor is 210 A.
- How many joules of energy does the battery deliver to the motor each second?
 - What power, in watts, does the motor use?

55. 50 W bulb; $P = \frac{V^2}{R}$, so $R = \frac{V^2}{P}$; Therefore, the lower P is caused by a higher R .

56. If the resistance is doubled, the current is halved.
57. No effect. $V = IR$, so $I = V/R$, and if the voltage and the resistance are both doubled, the current will not change.

58. No. At 1.5 V, $R = 3.3 \times 10^4 \Omega$. At 3.0 V, $R = 120 \Omega$. A device that obeys Ohm's Law has a resistance that is independent of the applied voltage.

59. Yes, because the current is the same everywhere in this circuit.

60. The wire with the smaller resistance. $P = \frac{V^2}{R}$; smaller R produces larger power, P , dissipated in the wire, which produces thermal energy at a faster rate.

Mastering Problems

22.1 Currents and Circuits

Level 1

61. a. 18 W
b. 1.6×10^4 J
62. a. 1.5 A
b. 27 V
c. 41 W
d. 1.5×10^5 J
63. a. 3.0 A
b. 27 V
c. 81 W
d. 2.9×10^5 J

64. a. 0.50 A
b. 9.0 V
c. 4.5 W
d. 1.6×10^4 J

65. 9.6×10^2 W

66. 1.4×10^2 W

67. a. 6.0×10^1 W
b. 1.8×10^4 J

68. a. 2.5×10^3 J/s
b. 2.5×10^3 W

69. 19 A

70. a. 4.5 W
b. 3.0×10^3 J

71. 24 V

72. 6.0 V

73. 1.2×10^2

74. 5.0 A

Level 2

75. a. $R = 143 \Omega$, $R = 148 \Omega$, $R = 150 \Omega$, $R = 154 \Omega$, $R = 159 \Omega$, $R = 143 \Omega$, $R = 143 \Omega$, $R = 154 \Omega$, $R = 157 \Omega$, $R = 161 \Omega$
 b. See Solutions Manual.
 c. The resistance of the nichrome wire increases somewhat as the magnitude of the voltage increases, so the wire does not quite obey Ohm's law.
76. $V = 28 \text{ V}$; See Solutions Manual.
77. a. No. The voltage is increased by a factor of $\frac{9.0}{6.0} = 1.5$, but the current is increased by a factor of $\frac{75}{66} = 1.1$
 b. 0.40 W
 c. 0.68 W
78. $1.08 \times 10^5 \text{ J}$; $9.5 \times 10^4 \text{ J}$
79. a. $3.0 \times 10^2 \Omega$
 b. $6.0 \times 10^1 \Omega$
 c. 2.0 A

Level 3

80. a. 32Ω
 b. $1.2 \times 10^2 \Omega$
 c. No. Resistance depends on voltage.
81. $I = 2 \text{ A}$; See Solutions Manual.

22.2 Using Electricity

Level 1

82. $\$510/\text{kWh}$
83. 0.15 A
84. $1.2 \times 10^6 \text{ J}$

Level 2

85. a. 1.1 A
 b. 45 V
86. $\$216$
87. 12.9 A
88. a. $\$18/\text{kWh}$
 b. $\$0.02$

69. **Dryers** A 4200-W clothes dryer is connected to a 220-V circuit. How much current does the dryer draw?
70. **Flashlights** A flashlight bulb is connected across a 3.0-V potential difference. The current through the bulb is 1.5 A.
 a. What is the power rating of the bulb?
 b. How much electric energy does the bulb convert in 11 min?
71. **Batteries** A resistor of 60.0Ω has a current of 0.40 A through it when it is connected to the terminals of a battery. What is the voltage of the battery?
72. What voltage is applied to a $4.0\text{-}\Omega$ resistor if the current is 1.5 A ?
73. What voltage is placed across a motor with a $15\text{-}\Omega$ operating resistance if there is 8.0 A of current?
74. A voltage of 75 V is placed across a $15\text{-}\Omega$ resistor. What is the current through the resistor?
75. Some students connected a length of nichrome wire to a variable power supply to produce between 0.00 V and 10.00 V across the wire. They then measured the current through the wire for several voltages. The students recorded the data for the voltages used and the currents measured, as shown in **Table 22-2**.
 a. For each measurement, calculate the resistance.
 b. Graph I versus V .
 c. Does the nichrome wire obey Ohm's law? If not, for all the voltages, specify the voltage range for which Ohm's law holds.
76. A lamp draws a 66-mA current when connected to a 6.0-V battery. When a 9.0-V battery is used, the lamp draws 75 mA .
 a. Does the lamp obey Ohm's law?
 b. How much power does the lamp dissipate when it is connected to the 6.0-V battery?
 c. How much power does it dissipate at 9.0 V ?
77. **Lightbulbs** How much energy does a 60.0-W lightbulb use in half an hour? If the lightbulb converts 12 percent of electric energy to light energy, how much thermal energy does it generate during the half hour?
78. The current through a lamp connected across 120 V is 0.40 A when the lamp is on.
 a. What is the lamp's resistance when it is on?
 b. When the lamp is cold, its resistance is $1/5$ as great as it is when the lamp is hot. What is the lamp's cold resistance?
 c. What is the current through the lamp as it is turned on if it is connected to a potential difference of 120 V ?
79. The graph in **Figure 22-17** shows the current through a device called a silicon diode.
 a. A potential difference of $+0.70 \text{ V}$ is placed across the diode. What is the resistance of the diode?
 b. What is the diode's resistance when a $+0.60\text{-V}$ potential difference is used?
 c. Does the diode obey Ohm's law?

Voltage, V (volts)	Current, I (amps)	Resistance, $R = V/I$ (amps)
2.00	0.0140	_____
4.00	0.0270	_____
6.00	0.0400	_____
8.00	0.0520	_____
10.00	0.0630	_____
-2.00	-0.0140	_____
-4.00	-0.0280	_____
-6.00	-0.0390	_____
-8.00	-0.0510	_____
-10.00	-0.0620	_____

76. Draw a series circuit diagram to include a $16\text{-}\Omega$ resistor, a battery, and an ammeter that reads 1.75 A . Indicate the positive terminal and the voltage of the battery, the positive terminal of the ammeter, and the direction of conventional current.

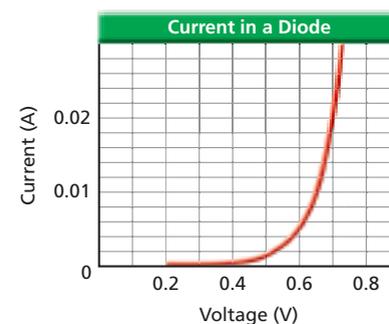


Figure 22-17

81. Draw a schematic diagram to show a circuit including a 90-V battery, an ammeter, and a resistance of 45Ω connected in series. What is the ammeter reading? Draw arrows showing the direction of conventional current.

22.2 Using Electric Energy

82. **Batteries** A 9.0-V battery costs $\$3.00$ and will deliver 0.0250 A for 26.0 h before it must be replaced. Calculate the cost per kWh.

612 Chapter 22 Current Electricity For more problems, go to Additional Problems, Appendix B.

Mixed Review

Level 1

89. 200 h
90. $2.2 \times 10^4 \text{ J}$
91. a. 2.5 A
 b. $2.3 \times 10^4 \text{ J}$


Level 2

92. a. 3.0 A
 b. 12 A
 c. The instant it is turned on.
93. The range is 10Ω to 600Ω .

Level 3


94. a. 5.0 A
 b. 40%

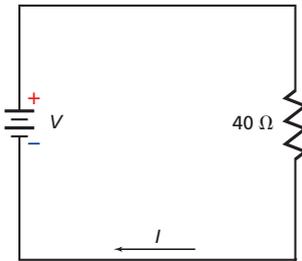83. What is the maximum current allowed in a 5.0-W, 220- Ω resistor?
84. A 110-V electric iron draws 3.0 A of current. How much thermal energy is developed in an hour?
85. For the circuit shown in **Figure 22-18**, the maximum safe power is 50 W. Use the figure to find the following:
- the maximum safe current
 - the maximum safe voltage



■ **Figure 22-18**

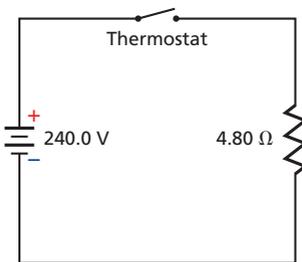86. **Utilities** **Figure 22-19** represents an electric furnace. Calculate the monthly (30-day) heating bill if electricity costs \$0.10 per kWh and the thermostat is on one-fourth of the time.



■ **Figure 22-19**

87. **Appliances** A window air conditioner is estimated to have a cost of operation of \$50 per 30 days. This is based on the assumption that the air conditioner will run half of the time and that electricity costs \$0.090 per kWh. Determine how much current the air conditioner will take from a 120-V outlet.
88. **Radios** A transistor radio operates by means of a 9.0-V battery that supplies it with a 50.0-mA current.
- If the cost of the battery is \$2.49 and it lasts for 300.0 h, what is the cost per kWh to operate the radio in this manner?
 - The same radio, by means of a converter, is plugged into a household circuit by a homeowner who pays \$0.12 per kWh. What does it now cost to operate the radio for 300.0 h?

Mixed Review

89. If a person has \$5, how long could he or she play a 200 W stereo if electricity costs \$0.15 per kWh?
90. A current of 1.2 A is measured through a 50.0- Ω resistor for 5.0 min. How much heat is generated by the resistor?
91. A 6.0- Ω resistor is connected to a 15-V battery.
- What is the current in the circuit?
 - How much thermal energy is produced in 10.0 min?
92. **Lightbulbs** An incandescent lightbulb with a resistance of 10.0 Ω when it is not lit and a resistance of 40.0 Ω when it is lit has 120 V placed across it.
- What is the current draw when the bulb is lit?
 - What is the current draw at the instant the bulb is turned on?
 - When does the lightbulb use the most power?
93. A 12-V electric motor's speed is controlled by a potentiometer. At the motor's slowest setting, it uses 0.02 A. At its highest setting, the motor uses 1.2 A. What is the range of the potentiometer?
94. An electric motor operates a pump that irrigates a farmer's crop by pumping 1.0×10^4 L of water a vertical distance of 8.0 m into a field each hour. The motor has an operating resistance of 22.0 Ω and is connected across a 110-V source.
- What current does the motor draw?
 - How efficient is the motor?
95. A heating coil has a resistance of 4.0 Ω and operates on 120 V.
- What is the current in the coil while it is operating?
 - What energy is supplied to the coil in 5.0 min?
 - If the coil is immersed in an insulated container holding 20.0 kg of water, what will be the increase in the temperature of the water? Assume 100 percent of the heat is absorbed by the water.
 - At \$0.08 per kWh, how much does it cost to operate the heating coil 30 min per day for 30 days?
96. **Appliances** An electric heater is rated at 500 W.
- How much energy is delivered to the heater in half an hour?
 - The heater is being used to heat a room containing 50 kg of air. If the specific heat of air is 1.10 kJ/kg \cdot $^{\circ}$ C, and 50 percent of the thermal energy heats the air in the room, what is the change in air temperature in half an hour?
 - At \$0.08 per kWh, how much does it cost to run the heater 6.0 h per day for 30 days?

95. a. 3.0×10^1 A
b. 1.1×10^6 J
c. 13° C
d. \$4.40

96. a. 9×10^5 J
b. 8° C
c. \$7

Thinking Critically

97. See Solutions Manual. Voltage:

$$V = \frac{\delta}{c} = \frac{5.0 \text{ C}}{1.0 \text{ F}} = 5.0 \text{ V}$$

Energy (area under curve):

$$E = \frac{1}{2} (5.0 \text{ V})(5.0 \text{ C}) = 13 \text{ J}$$

No. Graphically, total charge times final potential difference is exactly twice the area under the curve. Physically, it means that each coulomb would require the same maximum amount of energy to place it on the capacitor. Actually, the amount of energy needed to add each charge increases as each charge accumulates on the capacitor.

98. a. See Solutions Manual.
b. $\frac{\Delta T}{\Delta t} = \frac{1}{mC} \frac{\Delta Q}{\Delta t}$
c. 0.78° C/s
d. The kg unit cancels and the J unit cancels, leaving $^{\circ}$ C/s.
e. It might be possible to find a way to convert electrical energy to radiation using a different approach that would be more efficient. It might be possible to use a different frequency of electromagnetic radiation to improve conversion of microwave to thermal energy.
f. The conversion from microwave energy to thermal energy is good for water. It is not as good for other materials. The containers and dishes designed for use with microwave ovens convert little of the energy.

g. The empty oven means that the microwave energy has to be dissipated in the oven. This can lead to overheating of the oven components and to their failure.

99. a. In the case of heating a cup of water, an immersion heater uses resistance for energy conversion and is nearly 100 percent efficient. A microwave oven uses two energy conversions (electricity to microwave radia-

tion to heat) and is typically around 50 percent efficient.

b. In the case of heating a potato, a microwave oven heats mostly the potato and is more efficient than an electric oven or skillet, which also heats the air, cabinets, racks, and so on.

c. "It can be true but it depends on the specific application."

- 100.** The physical size of a resistor is determined by its power rating. Resistors rated at 100 W are much larger than those rated at 1 W.
- 101.** The volt-ampere graph for a resistor obeying Ohm's law is a straight line and is seldom necessary.
- 102.** Voltage-power and current-power; see Solutions Manual.

Writing in Physics

- 103.** The student's answer should include the idea that, for devices obeying Ohm's law, the voltage drop is proportional to current through the device and that the formula $R = V/I$, the definition of resistance, is a derivation from Ohm's law.
- 104.** Answers will vary, but students should determine that transmission lines can become hot enough to expand and sag when they have high currents. Sagging lines can be dangerous if they touch objects beneath them, such as trees or other power lines.

Cumulative Review

- 105.** 2.7×10^4 J/K; melting ice: 2.4×10^4 J/K
- 106.** 1.9 kPa or about 2/100 of the total air pressure
- 107.** 2.0 cm
- 108.** 1.4×10^{-4} m
- 109.** 0.41 N

Thinking Critically

- 97. Formulate Models** How much energy is stored in a capacitor? The energy needed to increase the potential difference of a charge, q , is represented by $E = qV$. But in a capacitor, $V = q/C$. Thus, as charge is added, the potential difference increases. As more charge is added, however, it takes more energy to add the additional charge. Consider a 1.0-F "supercap" used as an energy storage device in a personal computer. Plot a graph of V as the capacitor is charged by adding 5.0 C to it. What is the voltage across the capacitor? The area under the curve is the energy stored in the capacitor. Find the energy in joules. Is it equal to the total charge times the final potential difference? Explain.
- 98. Apply Concepts** A microwave oven operates at 120 V and requires 12 A of current. Its electric efficiency (converting AC to microwave radiation) is 75 percent, and its conversion efficiency from microwave radiation to heating water is also 75 percent.
- Draw a block power diagram similar to the energy diagram shown in Figure 22-2b on page 593. Label the function of each block according to total joules per second.
 - Derive an equation for the rate of temperature increase ($\Delta T/s$) from the information presented in Chapter 12. Solve for the rate of temperature rise given the rate of energy input, the mass, and the specific heat of a substance.
 - Use your equation to solve for the rate of temperature rise in degrees Celsius per second when using this oven to heat 250 g of water above room temperature.
 - Review your calculations carefully for the units used and discuss why your answer is in the correct form.
 - Discuss, in general terms, different ways in which you could increase the efficiency of microwave heating.
 - Discuss, in efficiency terms, why microwave ovens are not useful for heating everything.
 - Discuss, in general terms, why it is not a good idea to run microwave ovens when they are empty.
- 99. Analyze and Conclude** A salesclerk in an appliance store states that microwave ovens are the most electrically efficient means of heating objects.
- Formulate an argument to refute the clerk's claim. *Hint: Think about heating a specific object.*
 - Formulate an argument to support the clerk's claim. *Hint: Think about heating a specific object.*
 - Formulate a diplomatic reply to the clerk.

- 100. Apply Concepts** The sizes of 10- Ω resistors range from a pinhead to a soup can. Explain.
- 101. Make and Use Graphs** The diode graph shown in Figure 22-17 on page 612 is more useful than a similar graph for a resistor that obeys Ohm's law. Explain.
- 102. Make and Use Graphs** Based on what you have learned in this chapter, identify and prepare two parabolic graphs.

Writing in Physics

- 103.** There are three kinds of equations encountered in science: (1) definitions, (2) laws, and (3) derivations. Examples of these are: (1) an ampere is equal to one coulomb per second, (2) force is equal to mass times acceleration, (3) power is equal to voltage squared divided by resistance. Write a one-page explanation of where "resistance is equal to voltage divided by current" fits. Before you begin to write, first research the three categories given above.
- 104.** In Chapter 13, you learned that matter expands when it is heated. Research the relationship between thermal expansion and high-voltage transmission lines.

Cumulative Review

- 105.** A person burns energy at the rate of about 8.4×10^6 J per day. How much does she increase the entropy of the universe in that day? How does this compare to the entropy increase caused by melting 20 kg of ice? (Chapter 12)
- 106.** When you go up the elevator of a tall building, your ears might pop because of the rapid change in pressure. What is the pressure change caused by riding in an elevator up a 30-story building (150 m)? The density of air is about 1.3 kg/m^3 at sea level. (Chapter 13)
- 107.** What is the wavelength in air of a 17-kHz sound wave, which is at the upper end of the frequency range of human hearing? (Chapter 15)
- 108.** Light of wavelength 478 nm falls on a double slit. First-order bright bands appear 3.00 mm from the central bright band. The screen is 0.91 m from the slits. How far apart are the slits? (Chapter 19)
- 109.** A charge of $+3.0 \times 10^{-6}$ C is 2.0 m from a second charge of $+6.0 \times 10^{-5}$ C. What is the magnitude of the force between them? (Chapter 20)

614 Chapter 22 Current Electricity For more problems, go to Additional Problems, Appendix B.

EXAMVIEW® PRO


Use ExamView® Pro Testmaker CD-ROM to:

- Create **multiple versions** of tests.
- Create **modified** tests with one mouse click for **struggling** students.
- **Edit** existing questions and add your own questions.
- **Build** tests based on national curriculum standards.



Multiple Choice

- A 100-W lightbulb is connected to a 120-V electric line. What is the current that the lightbulb draws?
 - (A) 0.8 A
 - (B) 1 A
 - (C) 1.2 A
 - (D) 2 A
- A 5.0- Ω resistor is connected to a 9.0-V battery. How much thermal energy is produced in 7.5 min?
 - (A) 1.2×10^2 J
 - (B) 1.3×10^3 J
 - (C) 3.0×10^3 J
 - (D) 7.3×10^3 J
- The current in the flashlight shown below is 0.50 A, and the voltage is the sum of the voltages of the individual batteries. What is the power delivered to the bulb of the flashlight?
 - (A) 0.11 W
 - (B) 1.1 W
 - (C) 2.3 W
 - (D) 4.5 W

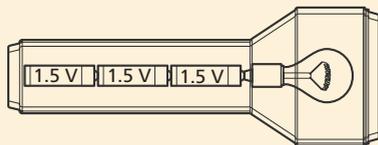


- If the flashlight in the illustration above is left on for 3.0 min, how much electric energy is delivered to the bulb?
 - (A) 6.9 J
 - (B) 14 J
 - (C) 2.0×10^2 J
 - (D) 4.1×10^2 J
- A current of 2.0 A flows through a circuit containing a motor with a resistance of 12 Ω . How much energy is converted if the motor runs for one minute?
 - (A) 4.8×10^1 J
 - (B) 2.0×10^1 J
 - (C) 2.9×10^3 J
 - (D) 1.7×10^5 J
- What is the effect on the current in a simple circuit if both the voltage and the resistance are reduced by half?
 - (A) divided by 2
 - (B) no change
 - (C) multiplied by 2
 - (D) multiplied by 4

- A 50.0- Ω resistance causes a current of 5.00 mA to flow through a circuit connected to a battery. What is the power in the circuit?
 - (A) 1.00×10^{-2} W
 - (B) 1.00×10^{-3} W
 - (C) 1.25×10^{-3} W
 - (D) 2.50×10^{-3} W
- How much electric energy is delivered to a 60.0-W lightbulb if the bulb is left on for 2.5 hours?
 - (A) 4.2×10^{-2} J
 - (B) 2.4×10^1 J
 - (C) 1.5×10^2 J
 - (D) 5.4×10^5 J

Extended Answer

- The diagram below shows a simple circuit containing a DC generator and a resistor. The table shows the resistances of several small electric devices. If the resistor in the diagram represents a hair dryer, what is the current in the circuit? How much energy does the hair dryer use if it runs for 2.5 min?

Device	Resistance (Ω)
Hair dryer	8.5 Ω
Heater	10.0 Ω
Small motor	12.0 Ω

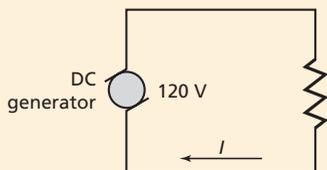

Test-Taking TIP

More Than One Graphic

If a test question has more than one table, graph, diagram, or drawing with it, use them all. If you answer based on just one graphic, you probably will miss an important piece of information.

Rubric

The following rubric is a sample scoring device for extended response questions.

Extended Response

Points	Description
4	The student demonstrates a thorough understanding of the physics involved. The response may contain minor flaws that do not detract from the demonstration of a thorough understanding.
3	The student demonstrates an understanding of the physics involved. The response is essentially correct and demonstrates an essential but less than thorough understanding of the physics.
2	The student demonstrates only a partial understanding of the physics involved. Although the student may have used the correct approach to a solution or may have provided a correct solution, the work lacks an essential understanding of the underlying physical concepts.
1	The student demonstrates a very limited understanding of the physics involved. The response is incomplete and exhibits many flaws.
0	The student provides a completely incorrect solution or no response at all.

Multiple Choice

- A
- D
- C
- D
- C
- B
- C
- D

Extended Answer

- $I = 14$ A; $E = 2.5 \times 10^5$ J